

ZLD-ASSIGNMENT 03


Name: Bilal Ahmed Khan

Sec: B ROLLNO: 20K-0183

PROGRAM: BS (CS)

QUESTION a:

Circuit Diagram:

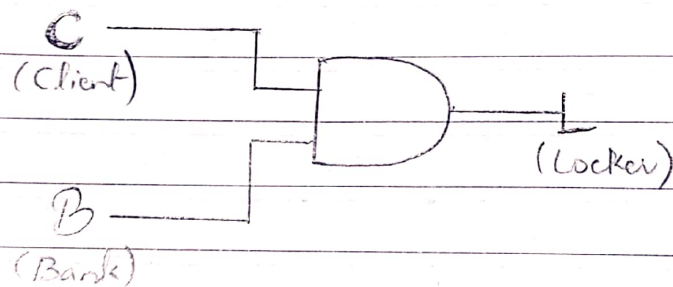

Truth Table:

| C | B | $C \cdot B = L$ | |
|---|---|-----------------|---------|
| 0 | 0 | 0 | (Close) |
| 0 | 1 | 0 | (Close) |
| 1 | 0 | 0 | (Close) |
| 1 | 1 | 1 | (Open) |


Mechanism:

When both keys i.e. (Client & Bank) are inserted the circuit gives a value of 1 (high) & the locker opens. Otherwise for all other conditions the locker remains closed since AND gate require all-highs as inputs to give ~~sof~~ output as 1.

QUESTION b

i) For NAND GATE: 

INPUTS:

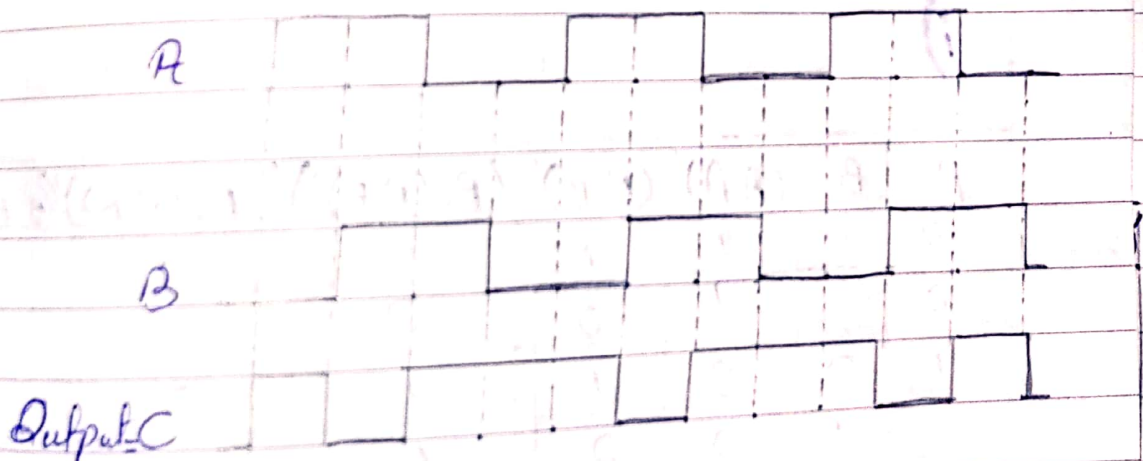

ii) FOR negative OR GATE:

INPUT:

A

B

OUTPUT:

C

1 — 1 — 1

QUESTION C:

i)

| A | B | $(A.A)'$ | $(B.B)'$ | $(B.(A.A)')'$ | $(A.(B.B)')'$ | $(B.(A.A)')' \cdot (A.(B.B)')'$ |
|---|---|----------|----------|---------------|---------------|---------------------------------|
| 0 | 0 | 1 | 1 | 1 | 1 | 0 |
| 0 | 1 | 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 0 | 1 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 | 1 | 0 |

For simplification:

$$= (B.(A.A)')' \cdot (A.(B.B)')'$$

Equivalent Circuit:

Date _____

$$= ((B.(A.A)')') \cdot ((A.(B.B)')')$$

By demorgan's law

$$(A.B)' = A' + B'$$


$$= ((B.(A.A)')') + ((A.(B.B)')')$$

$$\therefore A.A = A$$

$$= B.A' + A.B' = \text{XOR Gate}$$

Therefore the given circuit is equal to XOR gate

Equivalent circuit:

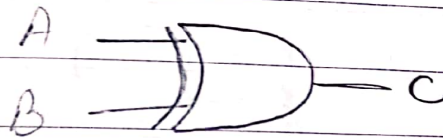

| ii) | A | B | (A.A)' | (B.B)' | ((A.A)'.(B.B)') |
|-----|---|---|--------|--------|-----------------|
| | 0 | 0 | 1 | 1 | 0 |
| | 0 | 1 | 1 | 0 | 1 |
| | 1 | 0 | 0 | 1 | 1 |
| | 1 | 1 | 0 | 0 | 1 |

Calculation on next page

Equivalent Circuit:

$$= ((A.A)' . (B.B)')' \quad (A.A)$$

$$= A.A = A$$

$$= (A'.B')' \quad (A.A)$$

$$= (A.B)' = A' + B'$$

$$= (A')' + (B')' \quad (A.A)$$

$$\boxed{A + B = \text{OR Gate}}$$

Hence OR gate is the equivalent of the given circuit.

Circuit diagram:



Date _____



| A | B | $(A+B)'$ | $(A+(A+B))'$ | $(B+(A+B))'$ | $((A+(A+B))' + (B+(A+B))')'$ | $((A+(A+B))' + (B+(A+B))')'$ |
|---|---|----------|--------------|--------------|------------------------------|------------------------------|
| 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 | 0 | 1 |
| 1 | 0 | 0 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 0 | 0 | 0 |

EQUIVALENT CIRCUIT:

$$= \left\{ (A + (A+B)')' + (B + (A+B)')' \right\}'$$
$$= \left\{ (A + (A+B)')' + (B + (A+B)')' \right\}'$$

$$A + A = A$$

$$= \left\{ \underbrace{(A + (A+B)')')}_A + \underbrace{(B + (A+B)')')}_B \right\}'$$

$$\therefore (A + B)' = A' \cdot B'$$

$$= \left[(A + (A+B)')' \right] \cdot \left[(B + (A+B)')' \right]$$


$$= (A + (A+B)') \cdot (B + (A+B)')$$

$$= (A + A'B') \cdot (B + A'B')$$

$$= A'B' + AB = \text{XNOR Gate}$$

Hence the equivalent of the given circuit is XNOR Gate

Equivalent circuit:-

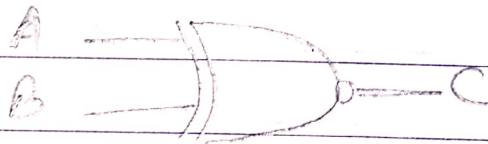

(iv)

| A | B | $(A.B)'$ | $A+B$ | $(A.B)'.(A+B)$ |
|---|---|----------|-------|----------------|
| 0 | 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 1 | 0 |

Equivalent circuit:

$$= (A.B)' . (A+B)$$

$$\therefore (A.B)' = A' + B'$$

$$= (A' + B') . (A+B)$$


$$= AA' + A'B + B'A + B'B'$$

$$\therefore AA' = 0$$

$$= AB' + BA' = \text{XOR Gate}$$


Hence the equivalent of the given circuit is ~~NOR~~ Gate
XOR

Equivalent circuit:

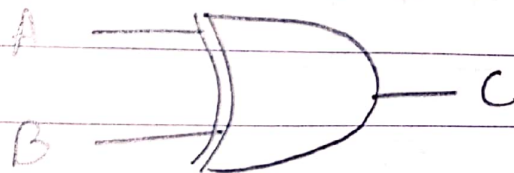


QUESTION d:



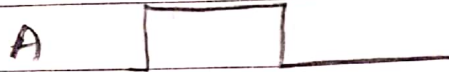
i) The waveform given in the question is incorrect the correct wave form is below



ii)

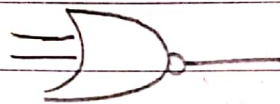

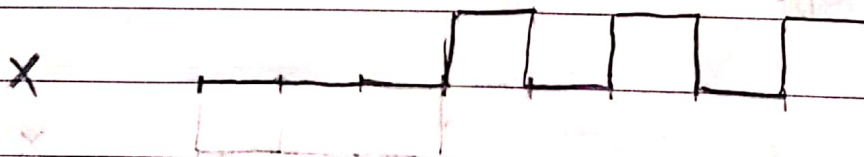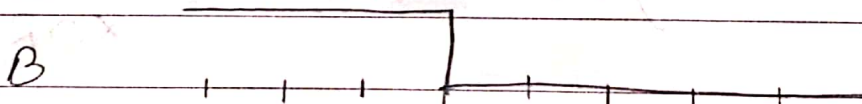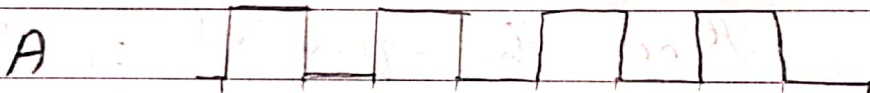The waveform in the question is incorrect the correct waveform is below.



iii)




Date _____



The waveform in the question is correct.

iv)

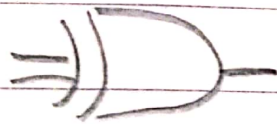

The waveform in the question is incorrect the correct waveform is below.

