

# Summary


## Multiplexers

A multiplexer (MUX) selects one data line from two or more input lines and routes data from the selected line to the output. The particular data line that is selected is determined by the select inputs.

Two select lines are shown here to choose any of the four data inputs.
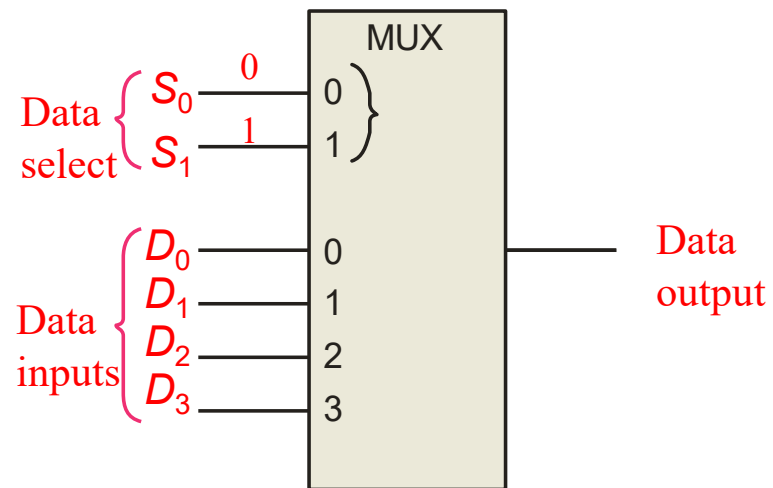
### Question

Which data line is selected if  $S_1S_0 = 10$ ?



For four input lines we need two Data-Select inputs. The combinations are given in table

**TABLE 6-8**


Data selection for a 1-of-4-multiplexer.

Data-Select Inputs		Input Selected
$S_1$	$S_0$	
0	0	$D_0$
0	1	$D_1$
1	0	$D_2$
1	1	$D_3$

**Task:**


Implement a Logic circuit for 4-input MUX

## Logic circuit for 4-input MUX

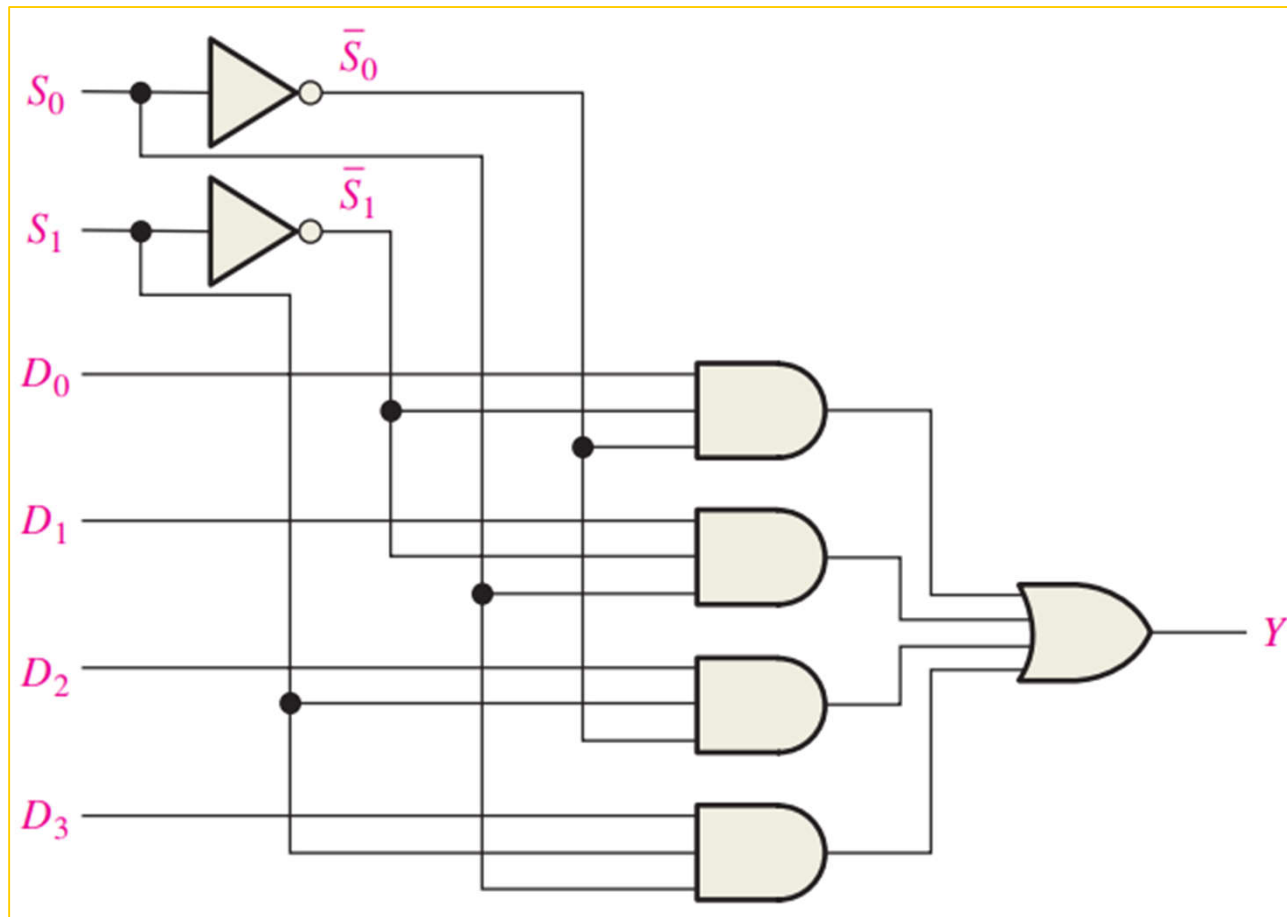

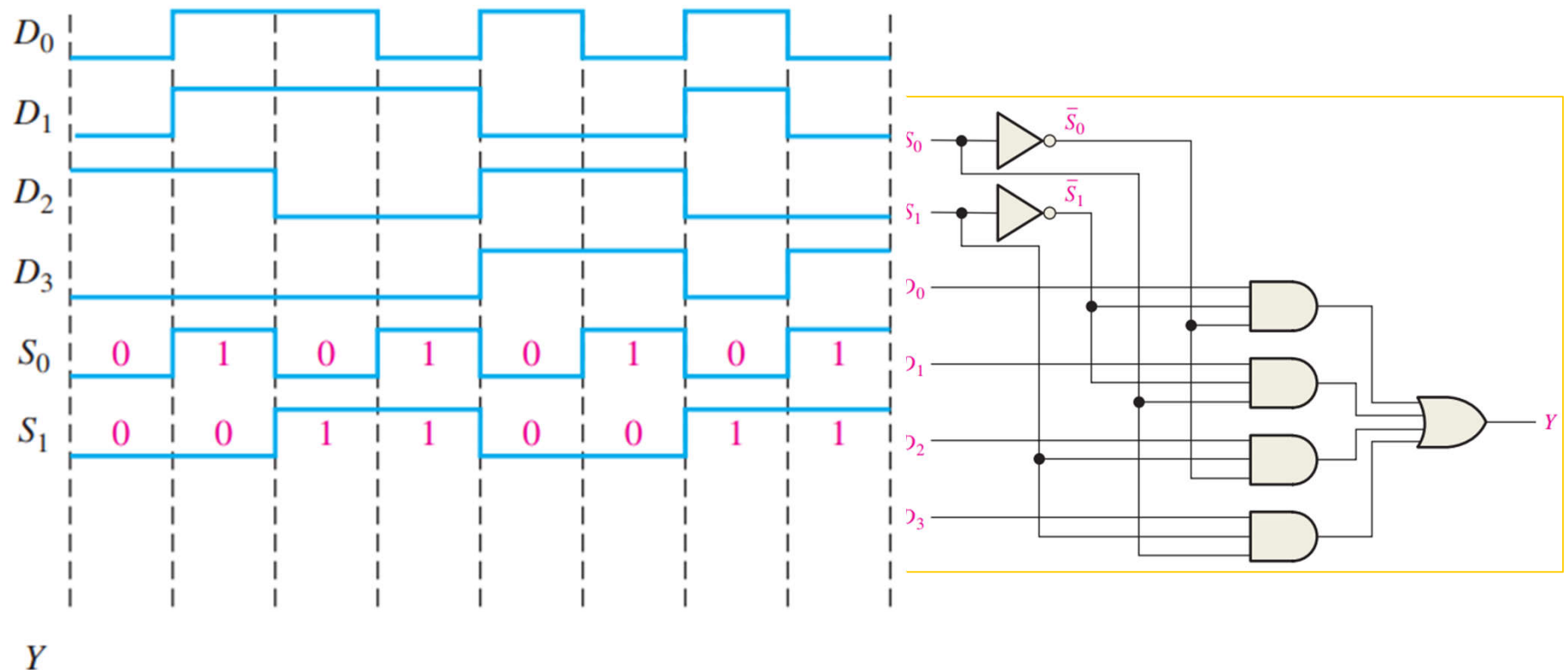
### EXAMPLE 6-14

The data-input and data-select waveforms in Figure 6-45(a) are applied to the multiplexer in Figure 6-44. Determine the output waveform in relation to the inputs.


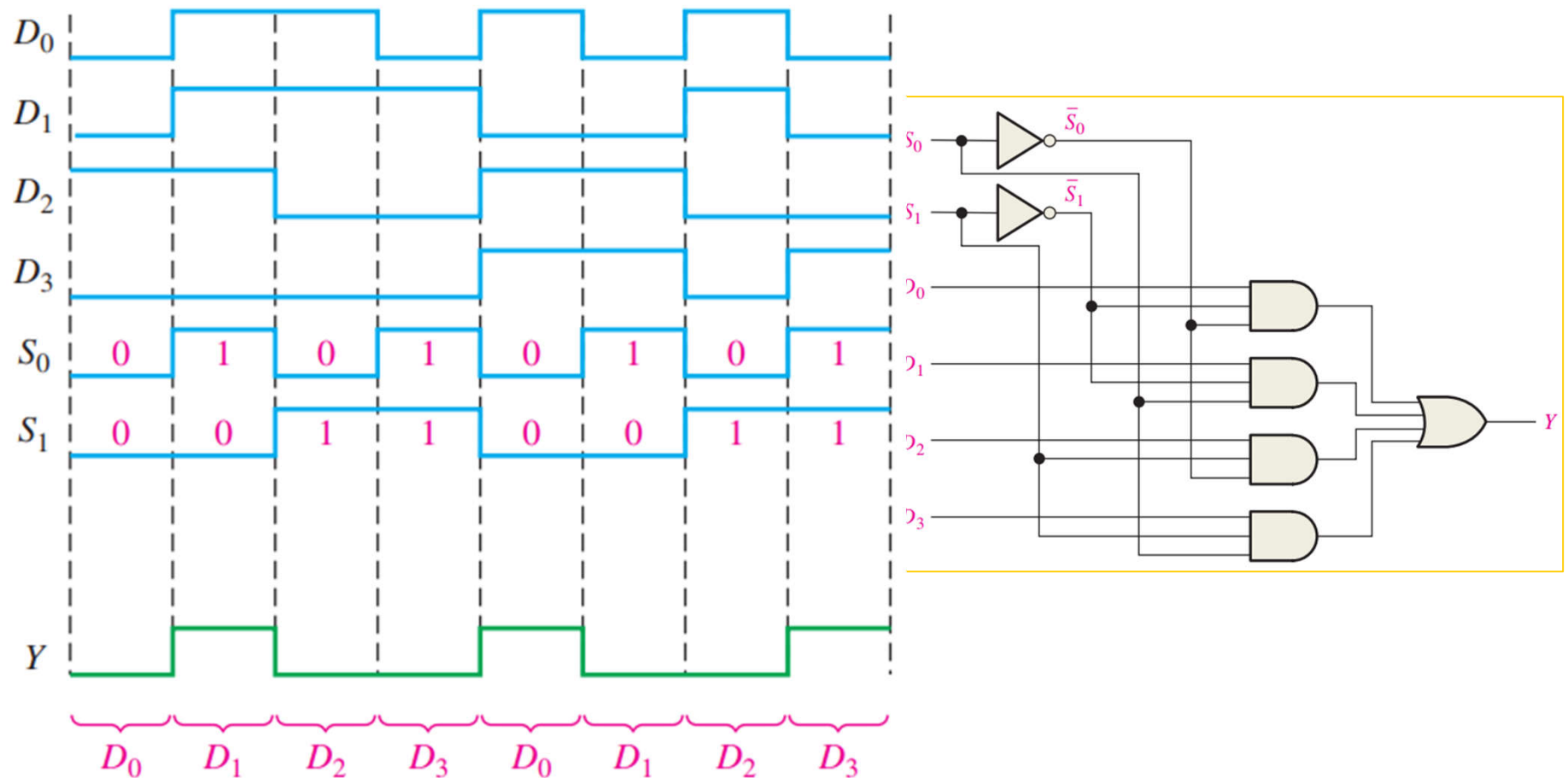
### EXAMPLE 6-14

The data-input and data-select waveforms in Figure 6-45(a) are applied to the multiplexer in Figure 6-44. Determine the output waveform in relation to the inputs.




# Summary
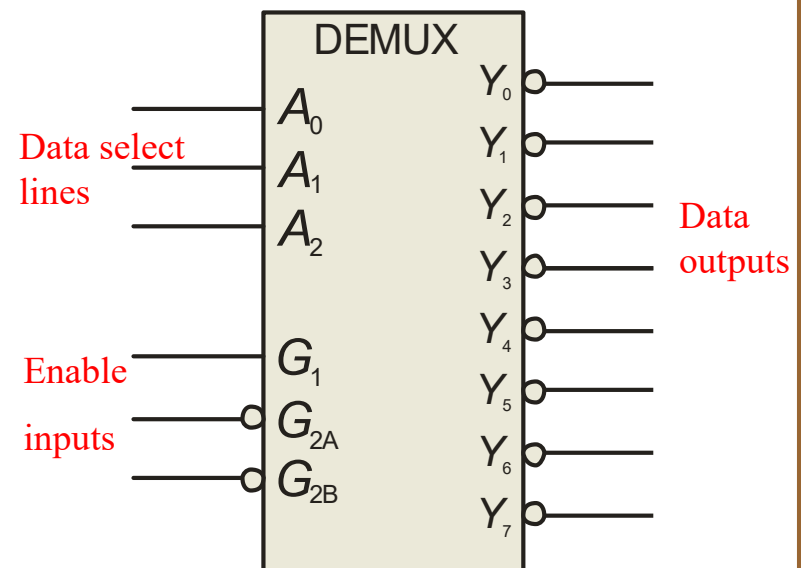
## Demultiplexers

A demultiplexer (DEMUX) performs the opposite function from a MUX. It switches data from one input line to two or more data lines depending on the select inputs.


The 74LS138 was introduced previously as a decoder but can also serve as a DEMUX. When connected as a DEMUX, data is applied to one of the enable inputs, and routed to the selected output line depending on the select variables. Note that the outputs are active-LOW as illustrated in the following example...



# Summary

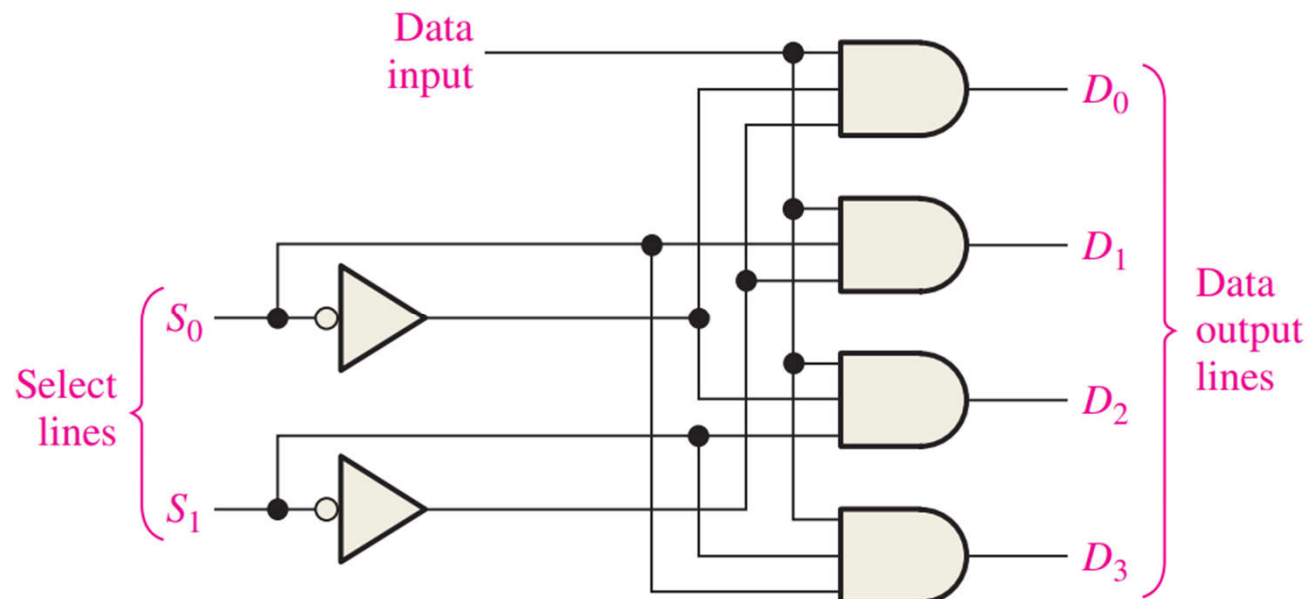
## Demultiplexers

A demultiplexer (DEMUX) performs the opposite function from a MUX. It switches data from one input line to two or more data lines depending on the select inputs.


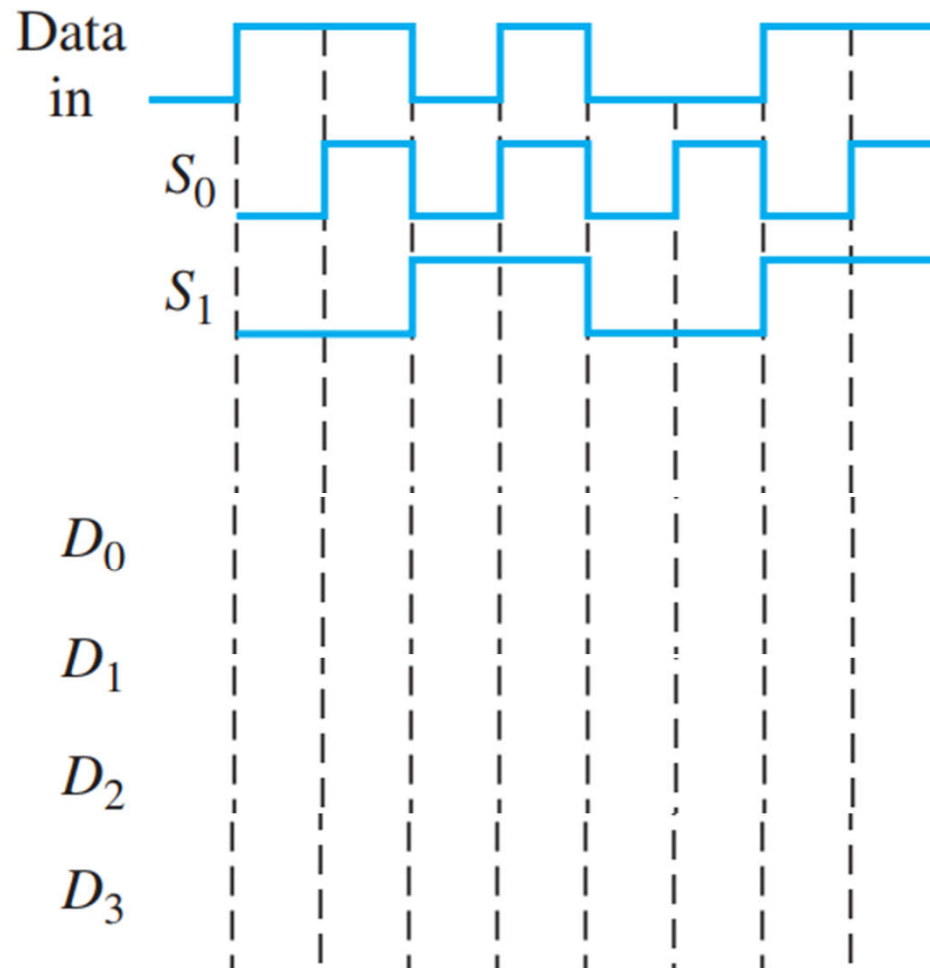
### EXAMPLE 6-18

The serial data-input waveform (Data in) and data-select inputs ( $S_0$  and  $S_1$ ) are shown in Figure 6-53. Determine the data-output waveforms on  $D_0$  through  $D_3$  for the demultiplexer in Figure 6-52.





### EXAMPLE 6-18

The serial data-input waveform (Data in) and data-select inputs ( $S_0$  and  $S_1$ ) are shown in Figure 6-53. Determine the data-output waveforms on  $D_0$  through  $D_3$  for the demultiplexer in Figure 6-52.

