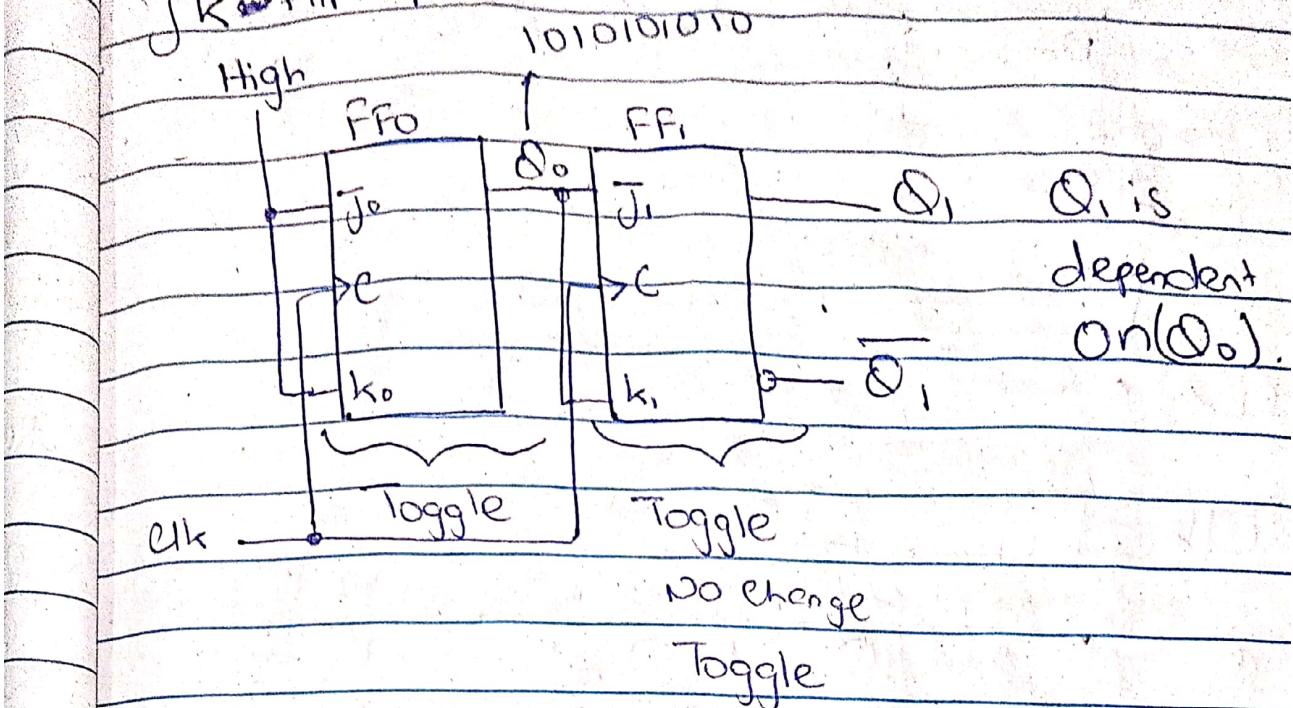


Chap 9

Synchronous Counters:-

Jk flip flop:-



Clk 0 | 1 | 0 | 1 | 0 | 1 |

Q_0 0 | 1 | 0 | 1 | 0 | 1 |

Toggle No change Toggle

Since Q_0 is passed in FF_1

so Q_0 is Toggle

Q_1 0 | 1 | 0 | 1 | 0 | 1 |

NC

Toggle

No change


Throughout

and because of

that FF_1 be Output Q_1 become Toggle
then No change then toggle.

When Q_0 is 1, Q_1 is toggle in next clock trigger and when Q_0 is 0, Q_1 remains same (No change) in next clock pulse

D flip-flop:-

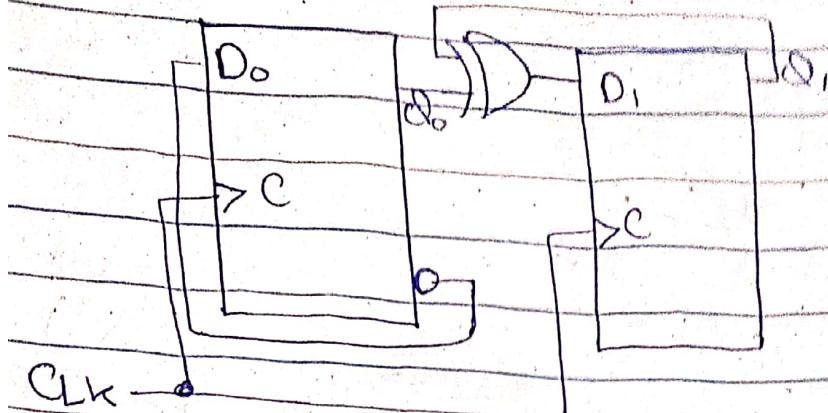

Q ₀	0	1	0	1	0	1
Q ₁	0	0	1	1	0	0

Annotations: 'no change' points to the first two columns of Q₀. 'Toggle' points to the third column of Q₀. 'per change' points to the fourth column of Q₀. 'Toggle' points to the fifth column of Q₀. 'no change in Q₁' points to the last two columns of Q₁.

3 bit Synchronous Counter:-

Clock pulse	Q ₂	Q ₁	Q ₀	
Initially	0	0	0	When Q ₀
1	0	0	1	and Q ₁ are
2	0	1	0	1 Q ₂ Toggle
3	0	1	1	
4	1	0	0	
5	1	0	1	
6	1	1	0	
7	1	1	1	


8 (recycles) 0 0 0

For 4 bit Synchronous Counter :-


Q_3, Q_2, Q_1, Q_0

(So Q_3 changes state when
 Q_2, Q_1, Q_0 are 1) And Q_2

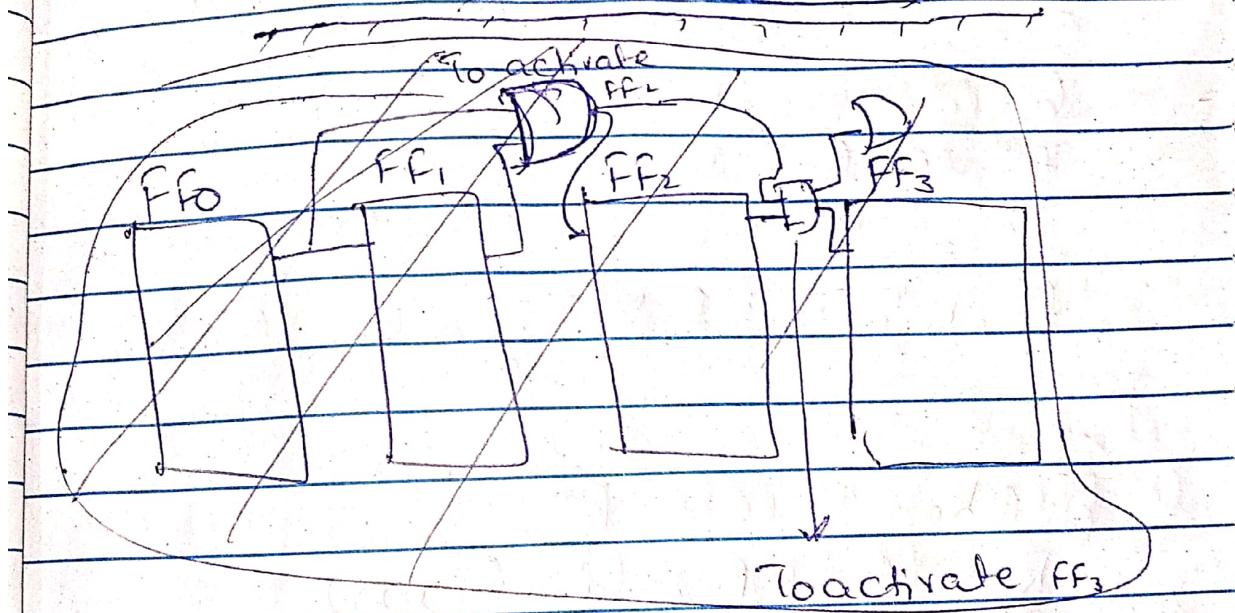changes state when Q_1, Q_0 are
1) And Q_1 changes state
when Q_0 is 1)


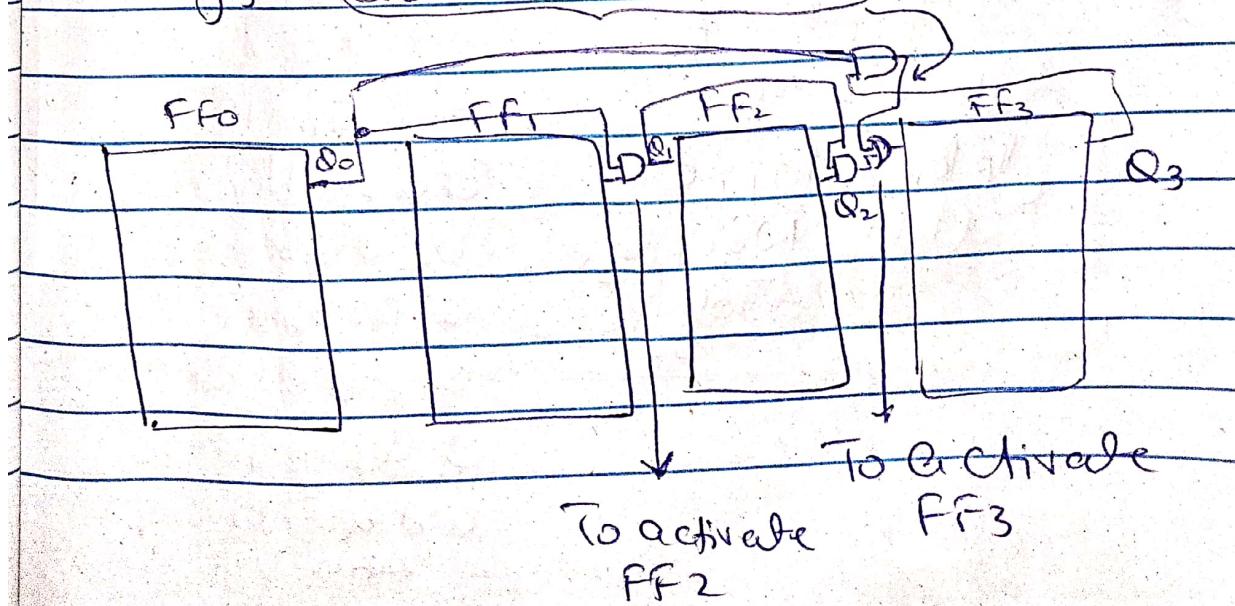
$$J_3 = \underbrace{Q_0 Q_1 Q_2 + Q_0 Q_2}_{\text{To activate } FF_3}$$



Up-Down Sequence for a 3 bit Counter

Clock pulse	UP	Q_2	Q_1	Q_0	Down
0		0	0	1	↑
1		0	0	1	↑
2		0	1	0	↑
3		0	1	1	↓
4		1	0	0	↑
5		1	0	1	↑
6		1	1	0	↑
7		1	1	1	↑

0, 1, 2, 3, 4, 5, 4, 3, 2, 3, 4, 5, 6, 7, 6, etc
Down

$$\bar{J}_0 = k_0 = 1$$

$$J_1 = k_1 = (Q_0 \cdot UP) + (\bar{Q}_0 \cdot Down)$$

$$J_2 = k_2 = (Q_0 \cdot Q_1 \cdot UP) + (\bar{Q}_0 \cdot \bar{Q}_1 \cdot Down)$$

$J_F = k_1 = \text{Toggle}$
 No change
 Toggle

when Q_1 and Q_0

are 1 Q_2 goes
up and becomes

1. And when


Q_1 and Q_0 are
0, Q_2 goes down
and becomes
zero

Since:-

$$\overline{J_0} = k_0 = 1$$

$$\bar{J}_1 = k_1 = (\bar{Q}_0 \cdot UP) + (\bar{Q}_0 \cdot Down)$$
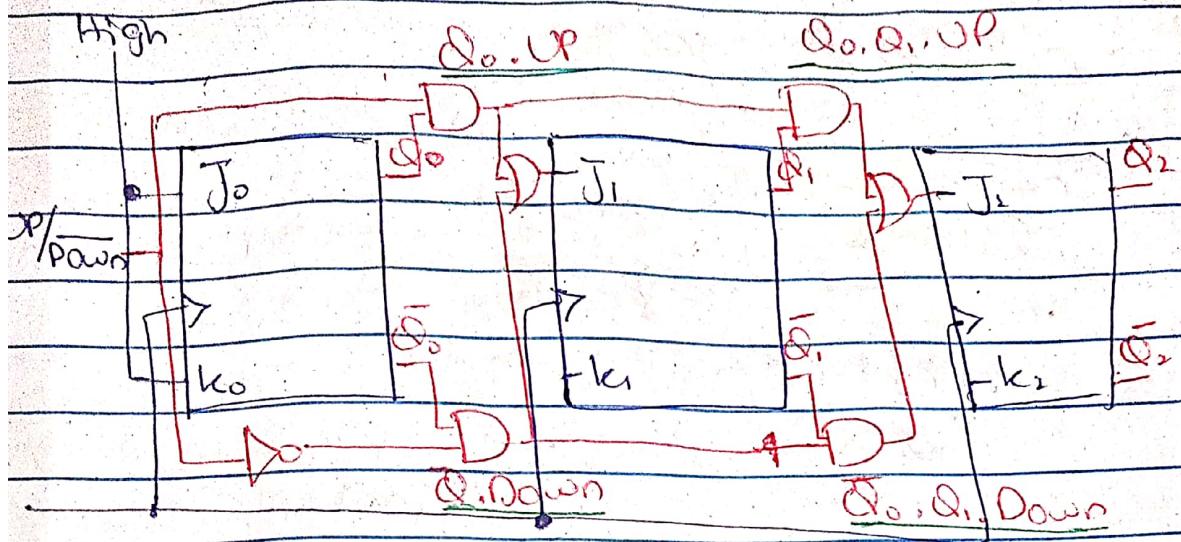
$$J_2 = k_2 = (Q_0, Q_1, UP) + (Q_0, \bar{Q}_1, Down)$$



Decoding:-

For decoding the three ffs will be \otimes outputs (Q) will be joined to AND in decimal combination like

To decode 6


$$Q_2 Q_1 \bar{Q}_0 \text{ must be AND}$$

$$1 \ 1 \ 0 = 6$$

Designing of Synchronous Counters:-


For memory we use either J.K flip flop
or D-flip-flop.

Finite State Machine

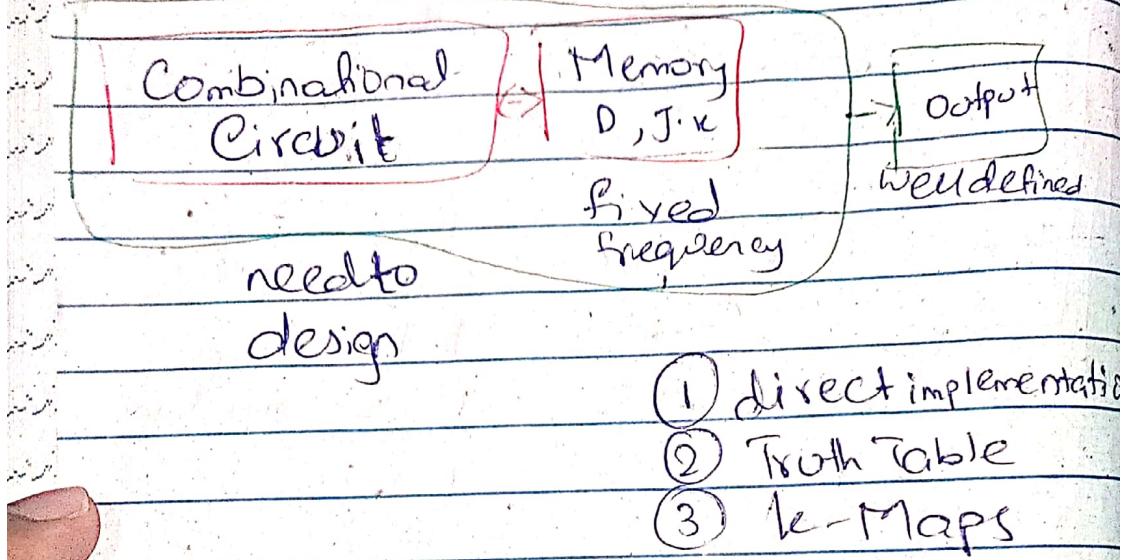

6 Steps To Create Asynchronous Counter

Step 1:- State Diagram

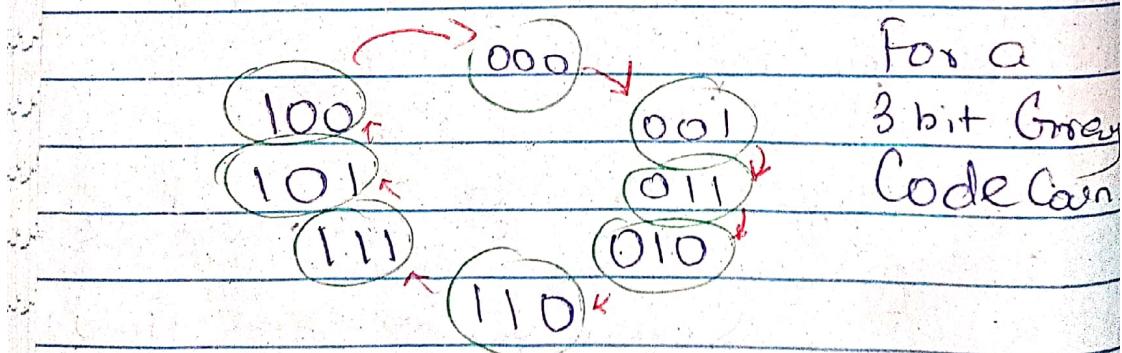

Step 2 : Next State Table

Present States	Next States
0 0 0	0 0 1
0 0 1	0 1 1
0 1 1	0 1 0
0 1 0	1 1 0
1 1 0	1 1 1
1 1 1	1 0 1
1 0 1	1 0 0
1 0 0	0 0 0

Step 3 :- Flip Flop Transition Table

Transition Table for a J-K FF:

Output Transitions		Flip-Flop Inputs	
Q_N	Q_{N+1}	J	k
0 → 0	0	0	*
0 → 1	1	1	*
1 → 0	0	*	1
1 → 1	1	*	0

Q_N : Present States

Q_{N+1} : next state

* : "don't care"

J	K	Clk	Q	\bar{Q}	
0	0	↑	0	1	No Change
0	1	↑	0	1	Reset
1	0	↑	1	0	Set
1	1	↑	Q _o	Q _o	Toggle

For D :- Flip-Flop Step 3

Output lenght Q _N	Q _{N+1}	Inputs D Reset	Inputs for 'D'
0	0	0	
0	1	1	
1	0	0	
1	1	1	

D	Clk	Q	
0	↑	0	Reset
1	↑	1	Set

Step 4: Karnaugh Maps

Transition Table			Next Table					
Output Transition	Flip-Flop Inputs		Present State			Next State		
	Q_2	Q_1	Q_0	Q_2	Q_1	Q_0		
$Q_N \rightarrow Q_N$	J	K	0	0	0	0	0	1
$0 \rightarrow 0$	0	X	0	0	1	0	1	1
$0 \rightarrow 1$	1	X	0	1	1	0	1	0
$1 \rightarrow 0$	X	1	0	1	0	1	1	0
$1 \rightarrow 1$	X	0	1	1	0	1	1	1
				1	1	1	1	0
				1	0	1	1	0
				1	0	0	0	0

The Karnaugh maps for (J_0, K_0) , (J_1, K_1) , (J_2, K_2) will be mapped differently (i.e. different for J_0 and K_0). The states will be seen from the transition table and then the corresponding J and k will be plotted on Karnaugh map according to their Q_2, Q_1, Q_0 .

Like Q_0 was initially 0 and at next state it became 1. So according to transition table when Q goes from $0 \rightarrow 1$, $J=1$ and $k=x$. and so accordingly plot for Q_1 by looking at Q_1 Next State and same for Q_2 .

Plot these by yourself
for practice

$Q_2 Q_1 \backslash Q_0$	00	01	11	10	$Q_2 Q_1 \backslash Q_0$	00	01	11	10
00	1	X	X	X	$\rightarrow Q_2 Q_1$	X	1	X	X
01	0	X	X	X	$\rightarrow Q_2 Q_1$	(X)	1	X	X
11	1	X	X	X	$\rightarrow Q_2 Q_1$	X	1	X	X
10	0	X	X	X	$\rightarrow Q_2 Q_1$	X	1	X	X

J_0 Map K_0 Map

$Q_2 Q_1 \backslash Q_0$	00	01	11	10	$Q_2 Q_1 \backslash Q_0$	00	01	11	10
00	0	1	X	X	$\rightarrow Q_2 Q_0$	00	X	X	X
01	X	(X)	X	X	$\rightarrow Q_2 Q_0$	01	0	0	X
11	X	X	X	X	$\rightarrow Q_2 Q_0$	11	0	1	X
10	X	X	X	X	$\rightarrow Q_2 Q_0$	10	X	X	X

J_1 Map K_1 Map

$Q_2 Q_1 \backslash Q_0$	00	01	11	10	$Q_2 Q_1 \backslash Q_0$	00	01	11	10
00	0	0	0	0	$\rightarrow Q_1 Q_0$	00	(X)	X	X
01	1	0	0	0	$\rightarrow Q_1 Q_0$	01	X	X	X
11	X	X	X	X	$\rightarrow Q_1 Q_0$	11	0	0	0
10	X	X	X	X	$\rightarrow Q_1 Q_0$	10	1	0	0

J_2 Map K_2 Map

$\overline{Q_1 Q_0}$

Step 5:- logic expression for flip-flop inputs

$$\bar{J}_0 = Q_2 Q_1 + \bar{Q}_2 \bar{Q}_1 = Q_2 \oplus Q_1$$

$$\bar{J}_1 = \bar{Q}_2 Q_0$$

$$k_0 = Q_2 \bar{Q}_1 + \bar{Q}_2 Q_1 = Q_2 \oplus Q_1$$

$$\bar{J}_1 = \bar{Q}_2 Q_0$$

$$k_1 = Q_2 Q_0$$

$$\bar{J}_2 = Q_1 \bar{Q}_0$$

$$k_2 = \bar{Q}_1 \bar{Q}_0$$

Step 6: Counter Implementation

