

ASSIGNMENT # 4

Question # 1

(a)

C \ AB	00	01	11	10
0	1	0	1	1
1	1	2	0	

$$Eq^n : (A + C)(\bar{A} + \bar{B} + \bar{C})$$

(b)

Z XY	00	01	11	10
0	1	0	0	0
1	1	0	1	1

$$Eq^n : (X + \bar{Y})(\bar{X} + Z)$$

(c)

$$\rightarrow (A + B + C)(\bar{A} + \bar{B} + C)(A + \bar{B} + C)(A + B + \bar{C}) \\ (\bar{A} + B + \bar{C})(\bar{A} + \bar{B} + C)$$

C \ AB	00	01	11	10
0	0	0	0	
1	0	0	1	0

$$Eq^n : A(\bar{B} + C)(\bar{A} + B + \bar{C})$$

Question # 2

a) $(A + \bar{B} + C + \bar{D})(\bar{A} + B + \bar{C} + D)(\bar{A} + \bar{B} + \bar{C} + \bar{D})$

AB	CD	00	01	11	10
00	1	1	1	1	1
01	1	0	1	1	1
11	1	1	0	1	1
10	1	1	1	0	1

No simplification

b) ~~$(W + X + \bar{Y} + Z)(\bar{W} + X + \bar{Y} + \bar{Z})$~~
 ~~$(\bar{W} + X + Y + Z)(W + X + \bar{Y} + \bar{Z})$~~
 ~~$(W + \bar{X} + Y + \bar{Z})(W + \bar{X} + Y + Z)$~~
 ~~$(W + X + Y + \bar{Z})(\bar{W} + \bar{X} + \bar{Y} + \bar{Z})$~~
 ~~$(W + X + Y + Z)(W + X + Y + \bar{Z})$~~

WX	YZ	00	01	11	10
00	0	0	0	0	0
01	1	0	0	1	1
11	1	1	0	1	1
10	1	1	0	0	0

Eq: $(W + X)(W + \bar{Z})(Y + \bar{Z})(\cancel{W} + X + Y)$

Question #3

a) $(A + \bar{B} + C)(A + \bar{B} + \bar{C})(A + B + \bar{C})(\bar{A} + \bar{B} + C)$

		AB	00	01	11	10
		C	0	0	0	1
			0	0	1	1
0	0		1	0	0	1
1	0		0	0	1	1

Eq: $\overline{BC} + AC$

b) ~~$(\bar{A} + B + C)(\bar{A} + \bar{B} + \bar{C})(\bar{A} + \bar{B} + C)$~~

$$\begin{aligned} & (\bar{A} + B + C + D)(\bar{A} + B + \bar{C} + \bar{D})(\bar{A} + B + \bar{C} + D)(\bar{A} + B + C + \bar{D}) \\ & (\bar{A} + \bar{B} + C + \bar{D})(\bar{A} + \bar{B} + \bar{C} + D)(A + B + \bar{C} + D) \\ & (A + \bar{B} + C + \bar{D}) \end{aligned}$$

		CD	00	01	11	10
		AB	00	01	11	10
			00	01	11	10
00	00		1	1	1	0
01	01		1	0	1	1
11	11		1	1	0	0
10	10		0	0	0	0

Eq: ~~$A\bar{B}C\bar{D}$~~ $\bar{A}\bar{C}\bar{D} + A\bar{B}\bar{C} + \bar{A}\bar{B}D + \bar{A}\bar{B}C$

Question #4

$$F(x,y,z) = \sum (1, 3, 7, 11, 15)$$

with $d(w, x, y, z) = \sum (0, 2, 5)$

WX	YZ	00	01	11	10
00	X	X	1	1	X
01	0	0	X	1	0
11	0	0	0	1	0
10	0	0	0	1	0

$$\text{Eq: } \bar{W}\bar{X} + \bar{W}Z + YZ$$

Question #5

a) $F(x,y,z) = \sum (0, 1, 2, 4, 5), d(x,y,z) = \sum (3, 6, 7)$

Z	XY	00	01	11	10
0	1	1	X	X	1
1	1	X	X	1	1

SOP: $\bar{Y} + \bar{X}Z$

POS: $(\bar{X} + Y)(\bar{Y} + Z)$

Z	XY	00	01	11	10
0	1	1	X	1	1
1	1	X	X	1	1

• POS

• SOP

- SOP: $\bar{Y} + \bar{X}Z$
- POS: $(\bar{X} + Y)(\bar{Y} + Z)$

b)

$\bar{A}B$	$C\bar{D}$	00	01	11	10
00	1	0	0	X	
01	X	0	1	1	
11	0	1	0	1	
10	1	X	0	X	

• SOP

• POS

• SOP: $\bar{B}\bar{D} + C\bar{D} + AB\bar{C}\bar{D}$

• POS: $(A + \bar{D})(\bar{B} + \bar{D})(\bar{C} + \bar{D})(\bar{B} + C + D)$

c)

$$F_{\neq}(A, B, C, D) = \sum(1, 3, 5, 7, 9, 15)$$

$$d(A, B, C, D) = \sum(4, 6, 12, 13)$$

$\bar{A}B$	$C\bar{D}$	00	01	11	10
00	0	1	1	0	
01	X	1	1	X	
11	X	X	1	0	
10	0	1	0	0	


• SOP

• POS

SOP: $\bar{A}\bar{B}D + \bar{C}D + B\bar{C} + BD$

POS: $D(\bar{A} + B + \bar{C})$

Question # 6

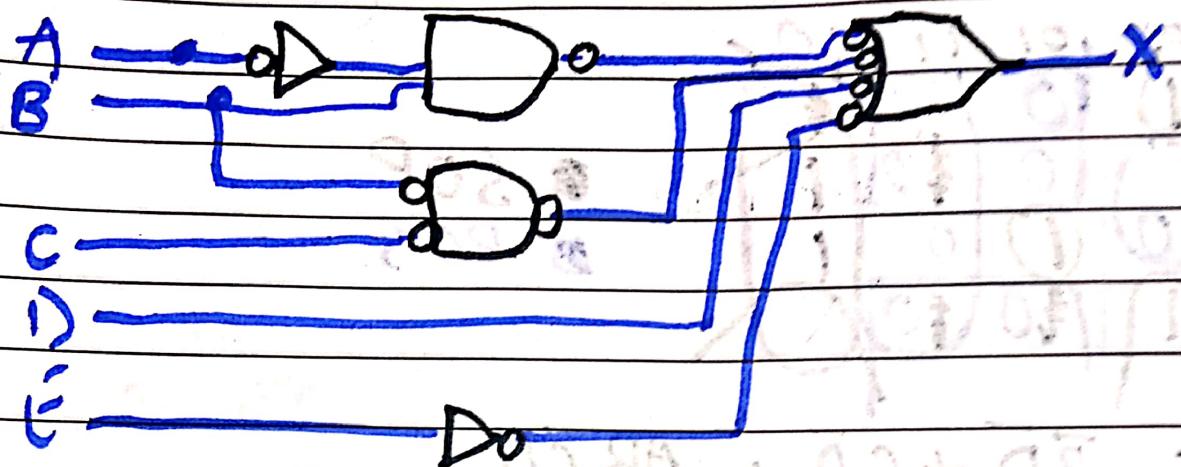


"When A is low and B is high,


Or when B and C are low,

Or when D is low, or when E is high,
output will be high".

Question # 7

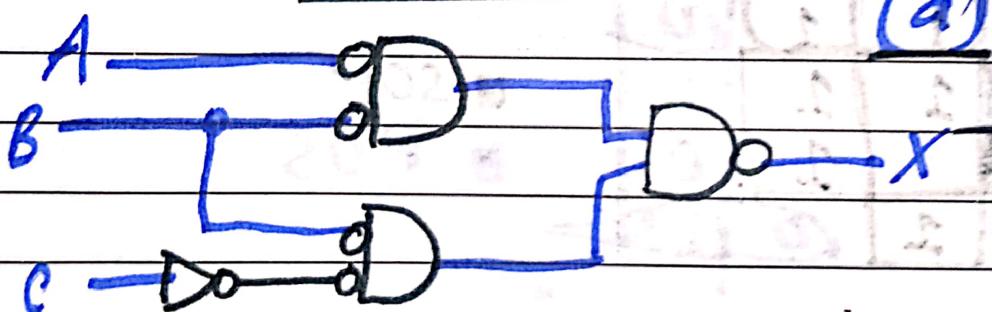


• For active-HIGH:

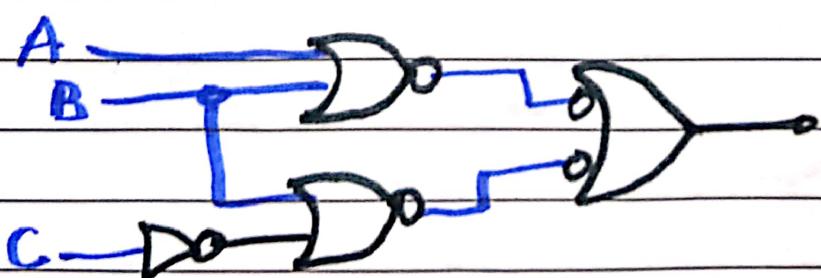


* "When A and B are low, and C is high", output will be low."

* "When A is high, or B is high or C is high, output will be low."


(6)

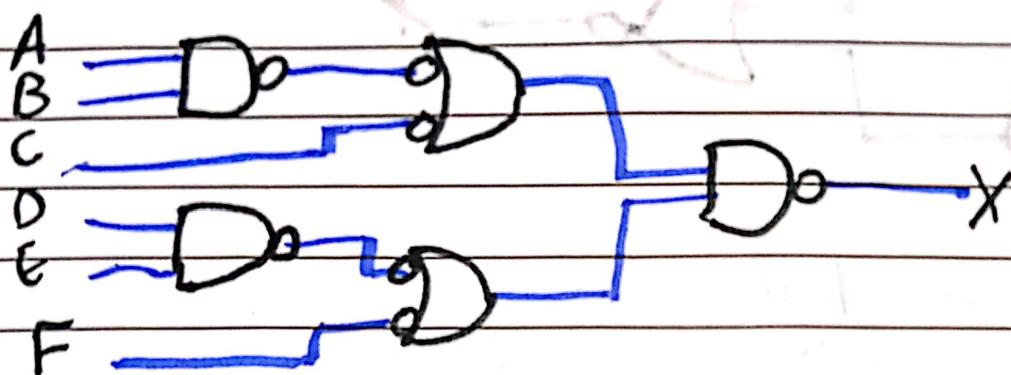Active - Low:


"When A, B, ~~C, E~~ are high or C is low,
and D, E are high or F is low, output is low"

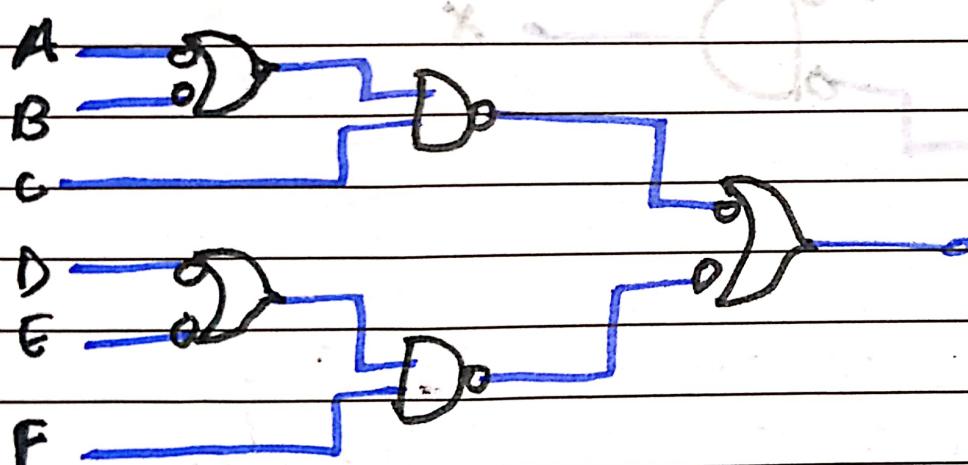Active - High:

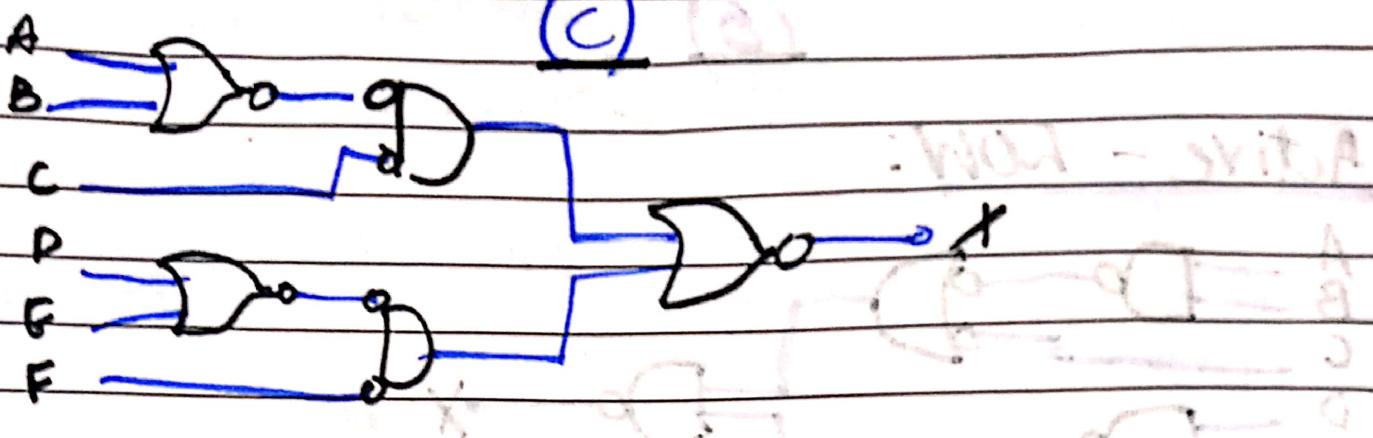"When A or B are low and C is high,
OR D or E are low and F is high,
output is high"



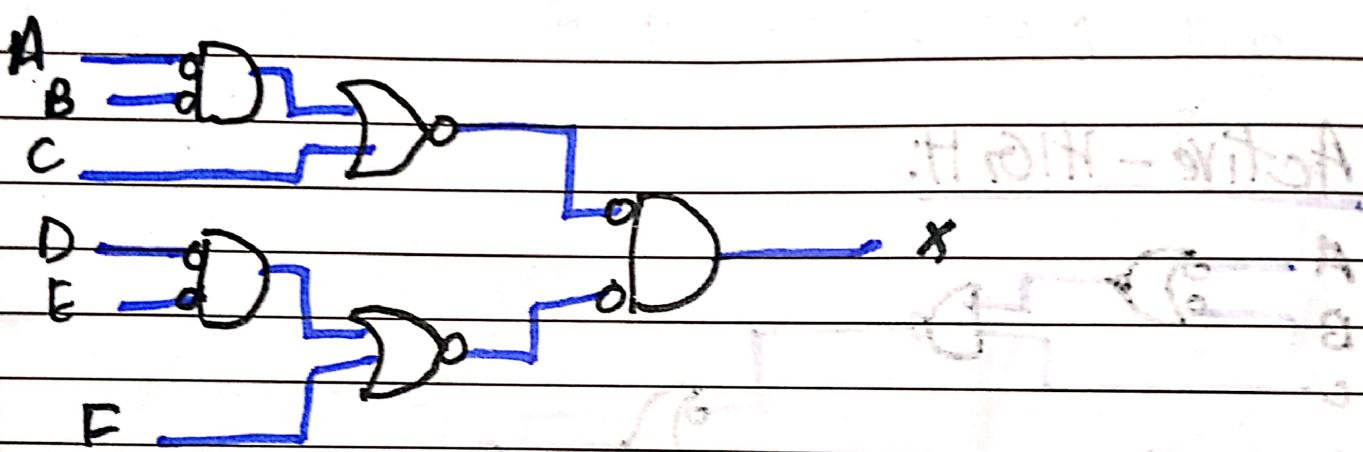"When A or B are high and C is low,
OR D or E are high and F is low,
output is 'low'!"



"When A and B are low or C is high,
AND D and E are low or F is high,
output is high."

Question #8

Eqn:

$$\cancel{A \cdot B} \quad AB(\overline{A} \cdot \overline{C}) + ABC = X$$

Simplification:


$$\Rightarrow AB(A+C) + ABC = X$$

$$\Rightarrow X = AB + ABC + ABC = X$$

$$X = \cancel{AB}(1+C) + ABC = A(\overline{B} + BC)$$

Hence: $X = A(\overline{B} + C)$ is the simplified version


Circuit:

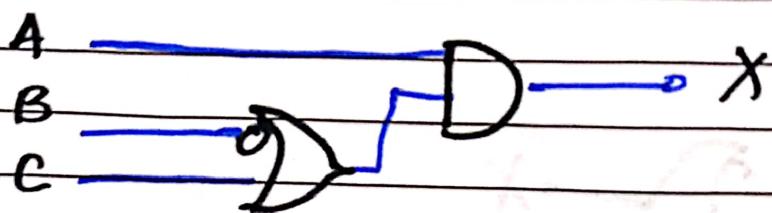

Question # 9


a) $(A+B)(C+D)=X$; no configuration required.

b) $X = \overline{ABC} + \overline{CD}$

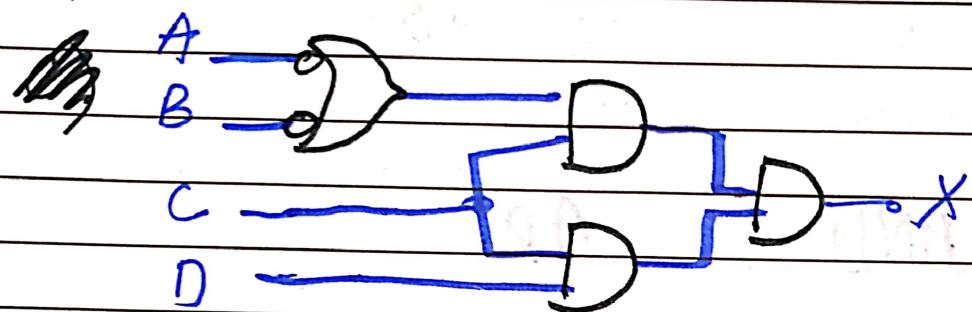


c) $X = (\overline{AB} + C)D + E$; no configuration required

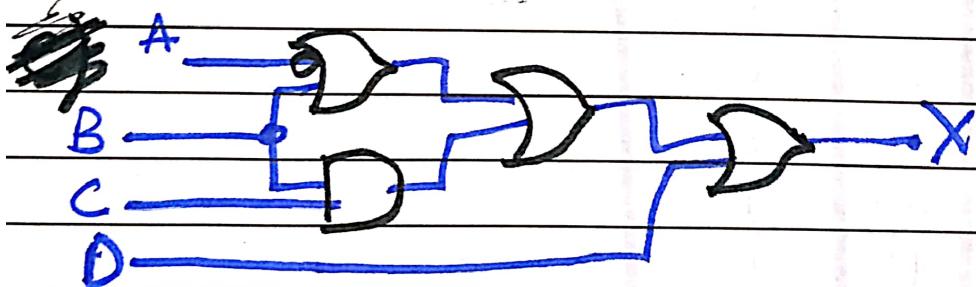
d) $X = (\overline{A} + \overline{B})\overline{CD} + D$



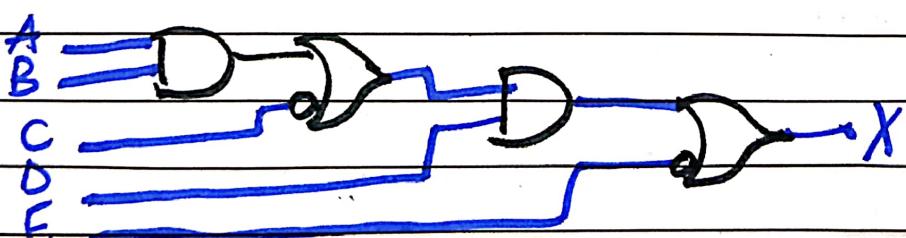e) $(\overline{AB} + \overline{C})D + \overline{E} = X$


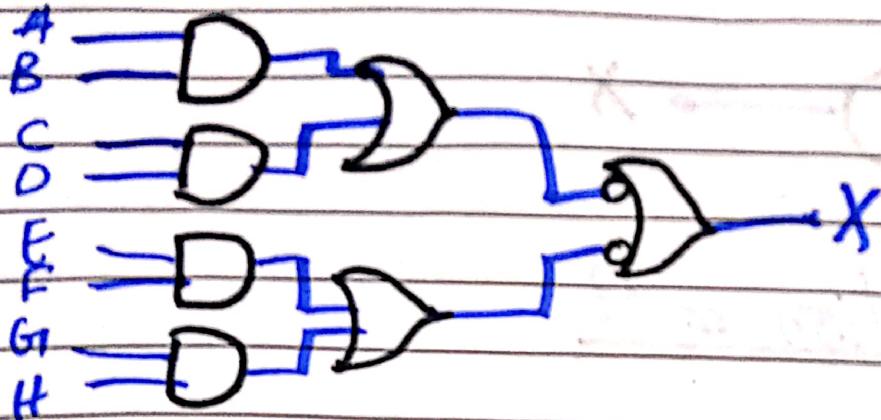
$$f) X = (\overline{AB} + \overline{CD})(\overline{EF} + \overline{GH})$$



Question # 10

a) Original circuit : eqⁿ : $AB + ABC$
 Simplified version : AB

$AB + ABC$ AND

AB :

A	B	C	AB	ABC	$AB + ABC$
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	0	0	0
0	1	1	0	0	0
1	0	0	0	0	0
1	0	1	0	0	0
1	1	0	1	0	1
1	1	1	1	1	1

Since, $AB = AB + ABC$

Therefore, verified!

b) Original Eqⁿ: $(\overline{AB} \cdot \overline{B+C}) + C = X$

Simplified version: $X = (\overline{AB} \cdot \overline{B+C}) \cdot \overline{C}$

or $X = (\overline{A} + \overline{B}) \overline{BC} \cdot \overline{C}$

or $X = \overline{A}\overline{B}\overline{C} + \overline{B}\overline{C}$

or $X = \overline{B}\overline{C}(\overline{A} + 1) = \overline{B}\overline{C} = \overline{B+C}$

Truth Table:

A	B	C	\overline{AB}	$\overline{B+C}$	$\overline{AB} \cdot \overline{B+C}$	$\overline{B+C}$
0	0	0	1	1	1	1
0	0	1	1	0	0	0
0	1	0	1	0	0	0
0	1	1	1	0	0	0
1	0	0	1	0	0	0
1	0	1	1	0	0	0
1	1	0	0	0	0	0
1	1	1	0	0	0	0

Since: $\overline{B+C} = [\overline{AB} (\overline{B+C})] + C$

Therefore, proved!

