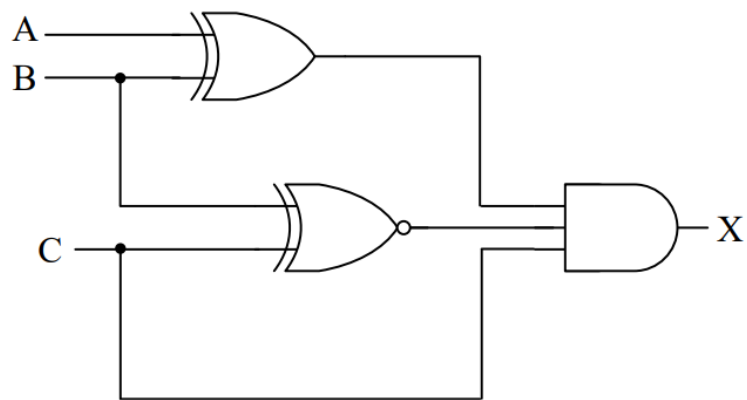


For the logic circuit shown in the figure, the required input condition (A,B,C) to make the output X = 1 is?



Write down the logic expression after each gate and finally for the complete circuit.

