

Assignment- 3

1. Determine the output, X , for a 2-input AND gate with the input waveforms shown in Figure-1. Show the proper relationship of output to inputs with a timing diagram. Repeat for 2 input OR gate.

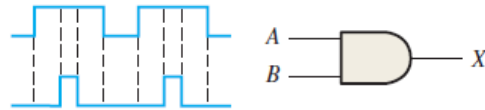


Fig-1

2. The waveforms in Figure-2 are applied to points A and B of a 2-input AND gate followed by an inverter. Draw the output waveform.

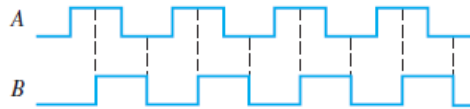


Fig-2

3. Considering (Figure -2) A and B as two inputs, draw the output for 2 input OR gate, NOR gate, NAND gate, Exclusive OR, and Exclusive NOR.
4. The input waveforms applied to a 3-input AND gate are as indicated in Figure 3. Show the output waveform in proper relation to the inputs with a timing diagram. Repeat for 3 input OR gate

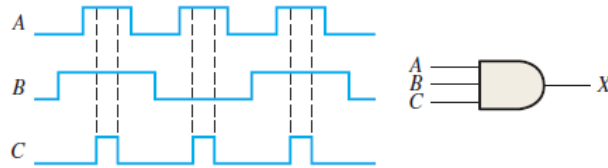


Fig-3

5. The input waveforms applied to a 4-input AND gate are as indicated in Figure 4. The output of the AND gate is fed to an inverter. Draw the net output waveform of this system. Repeat for 4 input OR gate.

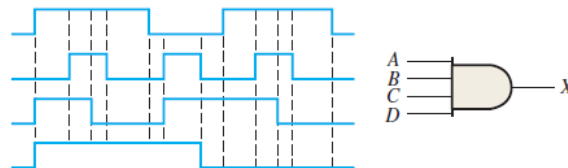


Fig-4

6. For the waveforms given in Figure 5, A and B are ANDed with output F , D and E are ANDed with output G , and C , F , and G are ORed. Draw the net output waveform.

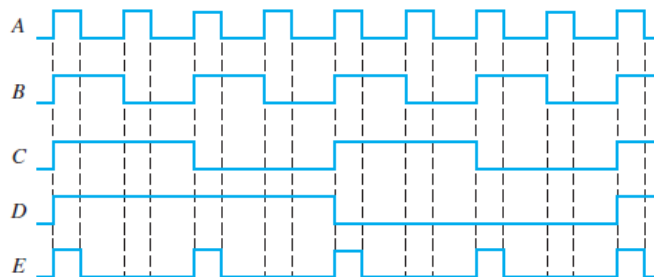


Fig-5

7. Show the truth table for a system of a 3-input OR gate followed by an inverter. For the set of input waveforms in Figure 6, determine the output for the gate shown and draw the timing diagram.

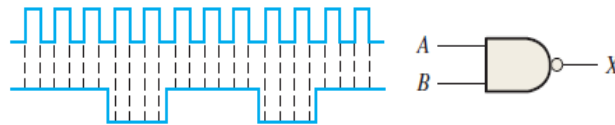


Fig-6

8. Determine the gate output for the input waveforms in Figure 7 and draw the timing diagram.

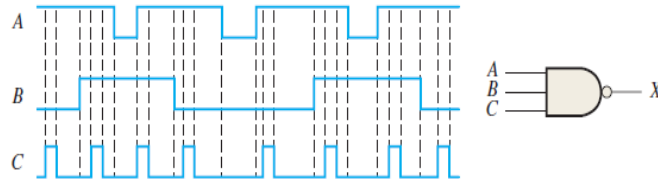


Fig-7

9. As you have learned, the two logic symbols shown in Figure 8 represent equivalent operations. The difference between the two is strictly from a functional viewpoint. For the NAND symbol, look for two HIGHS on the inputs to give a LOW output. For the negative-OR, look for at least one LOW on the inputs to give a HIGH on the output. Using these two functional viewpoints, show that each gate will produce the same output for the given inputs.

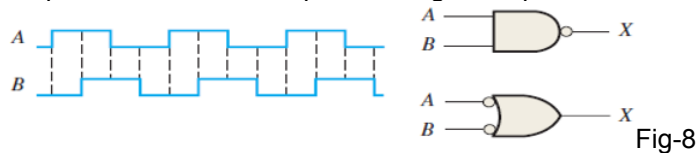


Fig-8

10. Determine the output waveform in Figure 9 and draw the timing diagram.

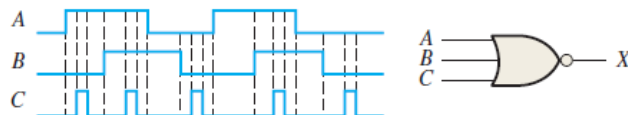


Fig-9

11. The NAND and the negative-OR symbols represent equivalent operations, but they are functionally different. For the NOR symbol, look for at least one HIGH on the inputs to give a LOW on the output. For the negative-AND, look for two LOWs on the inputs to give a HIGH output. Using these two functional points of view, show that both gates in Figure 3–88 will produce the same output for the given inputs.

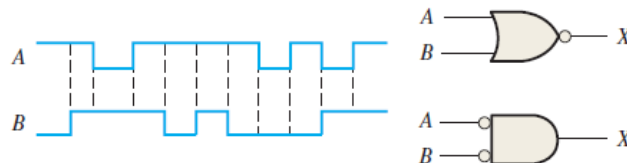


Fig-10

12. How does an exclusive-OR gate differ from an OR gate in its logical operation?
 13. Simplify the Boolean expressions:

(a) $x'y' + xy + x'y$

(b) $(x + y)(x + y')$

(c) $x'y + xy' + xy + x'y'$

(d) $x' + xy + xz' + xy'z'$

14. Simplify the Boolean expressions:

(a) $A'C' + ABC + AC'$

(b) $(x'y' + z)' + z + xy + wz$

(c) $A'B(D' + C'D) + B(A + A'CD)$

(d) $(A' + C)(A' + C')(A + B + C'D)$

15.

Simplify each of the following expressions using DeMorgan's theorems.

(a) $\overline{\overline{A}\overline{B}\overline{C}}$

(d) $\overline{\overline{A} + \overline{B}}$

(g) $\overline{\overline{\overline{A}(B + \overline{C})D}}$

(b) $\overline{\overline{A} + \overline{BC}}$

(e) $\overline{\overline{\overline{A}B}}$

(h) $\overline{(M + \overline{N})(\overline{M} + N)}$

(c) $\overline{\overline{\overline{A}BCD}}$

(f) $\overline{\overline{A} + \overline{C} + \overline{D}}$

(i) $\overline{\overline{ABCD}}$