

Assignment 5

[Due Date: 28 May]

Solve and submit the following questions as your assignment 5. Rest of the questions are for your practice.

[Assignment questions: 6,9,10,14,17,20,21,23,25]

1. If the waveforms in Figure 7-70 are applied to an active-HIGH S-R latch, draw the resulting Q output waveform in relation to the inputs. Assume that Q starts LOW.

 


FIGURE 7-70

2. Solve Problem 1 for the input waveforms in Figure 7-71 applied to an active-LOW $\bar{S} - \bar{R}$ latch.

 


FIGURE 7-71

3. Solve Problem 1 for the input waveform in Figure 7-72.



FIGURE 7-72

4. For a gated S-R latch, determine the Q and \bar{Q} outputs for the inputs in Figure 7-73. Show them in proper relation to the enable input. Assume that Q starts LOW.

 


FIGURE 7-73

5. Determine the output of a gated D latch for the inputs in Figure 7-74.



FIGURE 7-74

6. Determine the output of a gated D latch for the inputs in Figure 7-75.



FIGURE 7-75

9. The Q output of an edge-triggered D flip-flop is shown in relation to the clock signal in Figure 7-78. Determine the input waveform on the D input that is required to produce this output if the flip-flop is a positive edge-triggered type.

 


FIGURE 7-78

10. Draw the Q output relative to the clock for a D flip-flop with the inputs as shown in Figure 7-79. Assume positive edge-triggering and Q initially LOW.



FIGURE 7-79

11. Solve Problem 10 for the inputs in Figure 7-80.

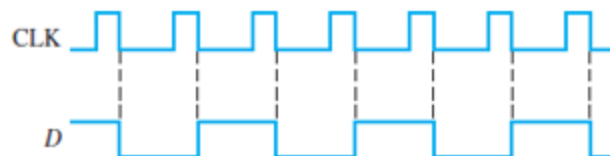


FIGURE 7-80

12. For a positive edge-triggered D flip-flop with the input as shown in Figure 7-81, determine the Q output relative to the clock. Assume that Q starts LOW.

 


FIGURE 7-81

13. Solve Problem 12 for the input in Figure 7-82.

 


FIGURE 7-82

14. Determine the Q waveform relative to the clock if the signals shown in Figure 7-83 are applied to the inputs of the J-K flip-flop. Assume that Q is initially LOW.

 


FIGURE 7-83

15. For a negative edge-triggered J-K flip-flop with the inputs in Figure 7-84, develop the Q output waveform relative to the clock. Assume that Q is initially LOW.


 



FIGURE 7-84

 16. The following serial data are applied to the flip-flop through the AND gates as indicated in Figure. Determine the resulting serial data that appear on the Q output. There is one clock pulse for each bit time. Assume that Q is initially 0 and that PRE and CLR are HIGH. Rightmost bits are applied first.


J_1 : 1010011
 J_2 : 0111010
 J_3 : 1111000
 K_1 : 0001110
 K_2 : 1101100
 K_3 : 1010101



 17. For the circuit in Figure -1, complete the timing diagram in Figure 2 by showing the Q output (which is initially LOW). Assume PRE and CLR remain HIGH.



 
18. Solve Problem 2 with the same J and K inputs but with the PRE and CLR inputs as shown in Figure 3 in relation to the clock.




19. Show how to connect a 4-bit asynchronous counter for each of the following moduli. Also for 30kHz clock determine the frequency at the output of each counter.

(a) 9 (b) 11 (c) 13 (d) 14 (e) 15

 20. A D flip-flop is connected as shown in Figure 7-90. Determine the Q output in relation to the clock. What specific function does this device perform?




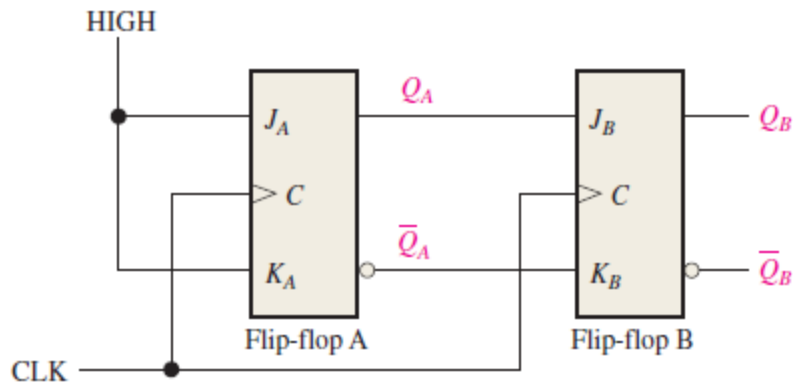21. For the circuit in Figure, develop a timing diagram for eight clock pulses, showing the QA and QB outputs in relation to the clock.




22. Show a complete timing diagram for a 3-bit up/down counter that goes through the following sequence. Indicate when the counter is in the UP mode and when it is in the DOWN mode. Assume positive edge-triggering. 0, 1, 2, 3, 2, 1, 2, 3, 4, 5, 6, 5, 4, 3, 2, 1, 0

 
23. **Develop** the Q output waveforms for a 74HC190 up/down counter with the input waveforms shown in Figure. A binary 0 is on the data inputs. Start with a count of 0000.



 24. **Determine** the sequence of the counter in Figure.



 25. **Determine** the sequence of the counter in Figure 9-74. Begin with the counter cleared.




26. Design a counter to produce the following sequence. Use J-K flip-flops. 00, 10, 01, 11, 00,

27. Design a counter to produce the following binary sequence. Use J-K flip-flops. 1, 4, 3, 5, 7, 6, 2, 1,

b.

28. Design a counter to produce the following binary sequence. Use J-K flip-flops. 0, 9, 1, 8, 2, 7, 3, 6, 4, 5, 0, ...

 29. Design a binary counter with the sequence shown in the state diagram of Figure. (using D flip flop)



i.

30. Design a counter by using D -flip flop only with the irregular binary count sequence shown in the state diagram of Fig. Include Next-state table, transition table, Karnaugh maps and final circuit.

