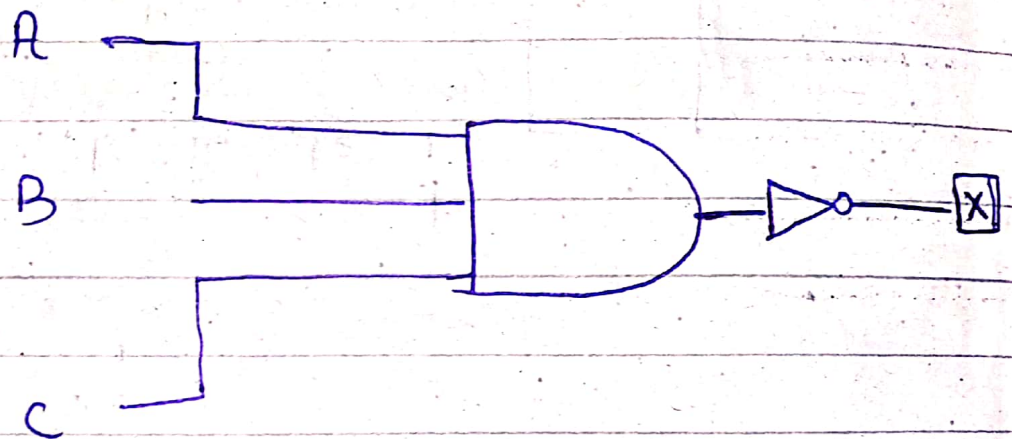



ASSIGNMENT #04

QUESTION A




QUESTION B

Boolean Expression: $A'B'C' + ABC$

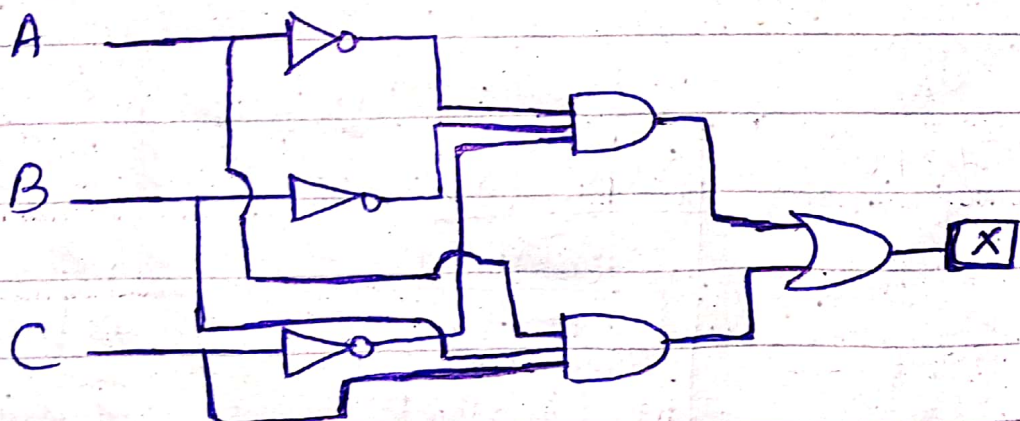


QUESTION C

i)

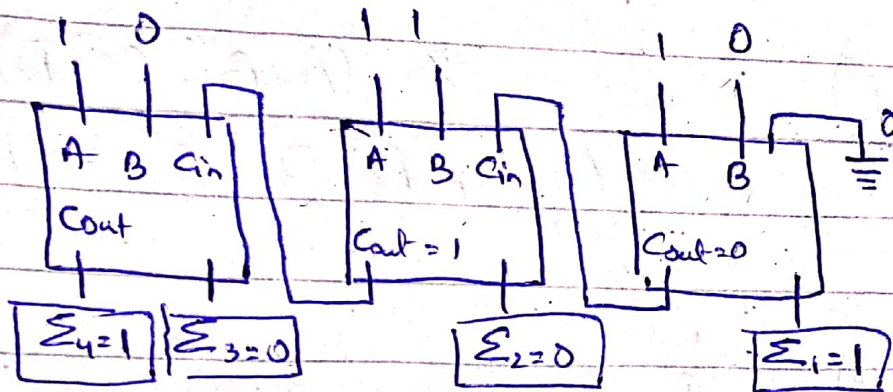


ii)

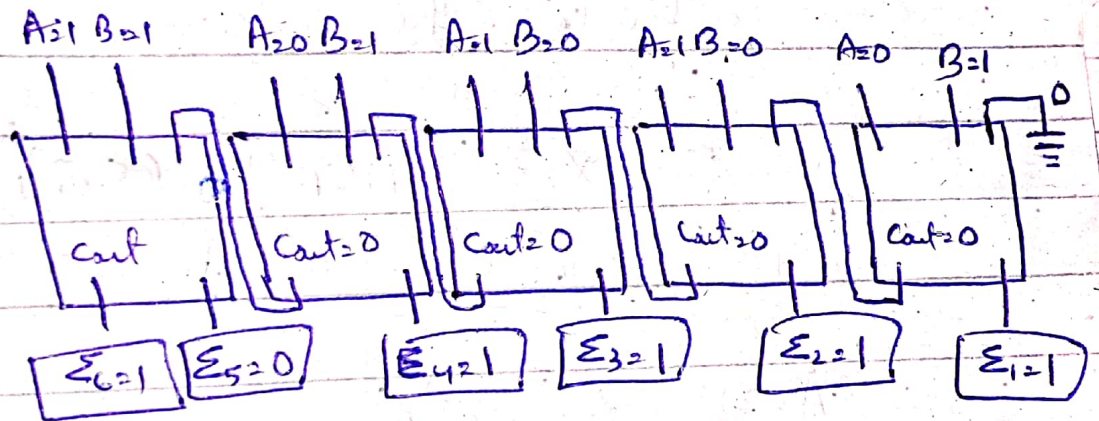

QUESTION. D

a) When K is HIGH the numbers are subtracted b/c of the condition ($\overline{\text{Add/Sub}}$)

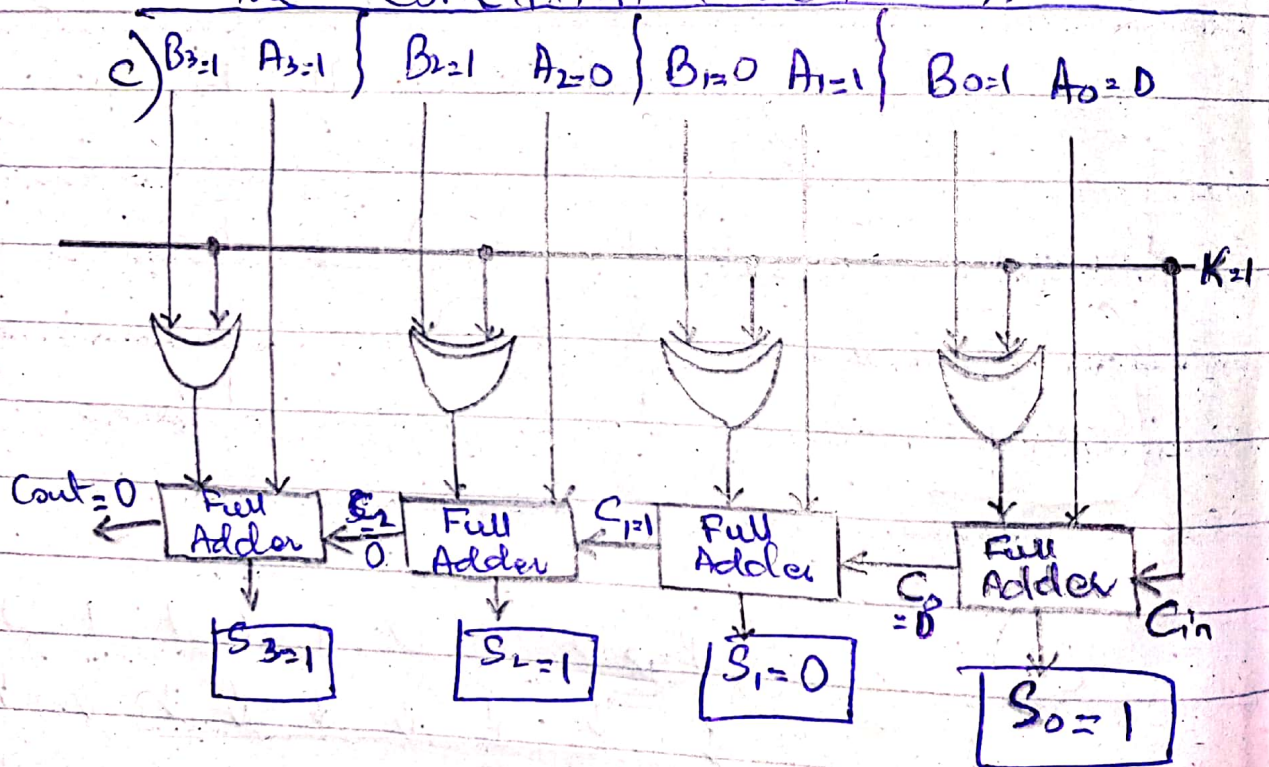b) When K is LOW the two numbers are added b/c of the condition ($\overline{\text{Add/Sub}}$).



QUESTION E:-

Logic To convert Binary to gray code:-

Following logic is implemented to convert Binary code to gray code.

Binary number = 0101

Binary = 0 \rightarrow 1 \rightarrow 0 \rightarrow 1
 ↓ ↓ ↓ ↓
Gray = 0 1 1 1


a) 1 0 1 0 1 1 1 1 0 0
 ↓ ↓ ↓ ↓ ↓ ↓ ↓ ↓ ↓ ↓
Gray = 1 1 1 1 1 0 0 0 1 0

b) 1 1 1 1 0 0 0 0 1 1
 ↓ ↓ ↓ ↓ ↓ ↓ ↓ ↓ ↓ ↓
Gray = 1 0 0 0 1 0 0 0 1 0


c) $\begin{matrix} 1 & 0 & 1 & 1 & 1 & 1 & 0 & 0 & 1 & 1 \\ \downarrow & \downarrow & \downarrow & \downarrow & \downarrow & \downarrow & \downarrow & \downarrow & \downarrow & \downarrow \\ \text{Gray} = 1 & 1 & 1 & 0 & 0 & 0 & 1 & 0 & 1 & 1 \end{matrix}$

d) $\begin{matrix} 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 \\ \downarrow & \downarrow & \downarrow & \downarrow & \downarrow & \downarrow & \downarrow & \downarrow & \downarrow & \downarrow \\ \text{Gray} = 1 & 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 \end{matrix}$

QUESTION F:-

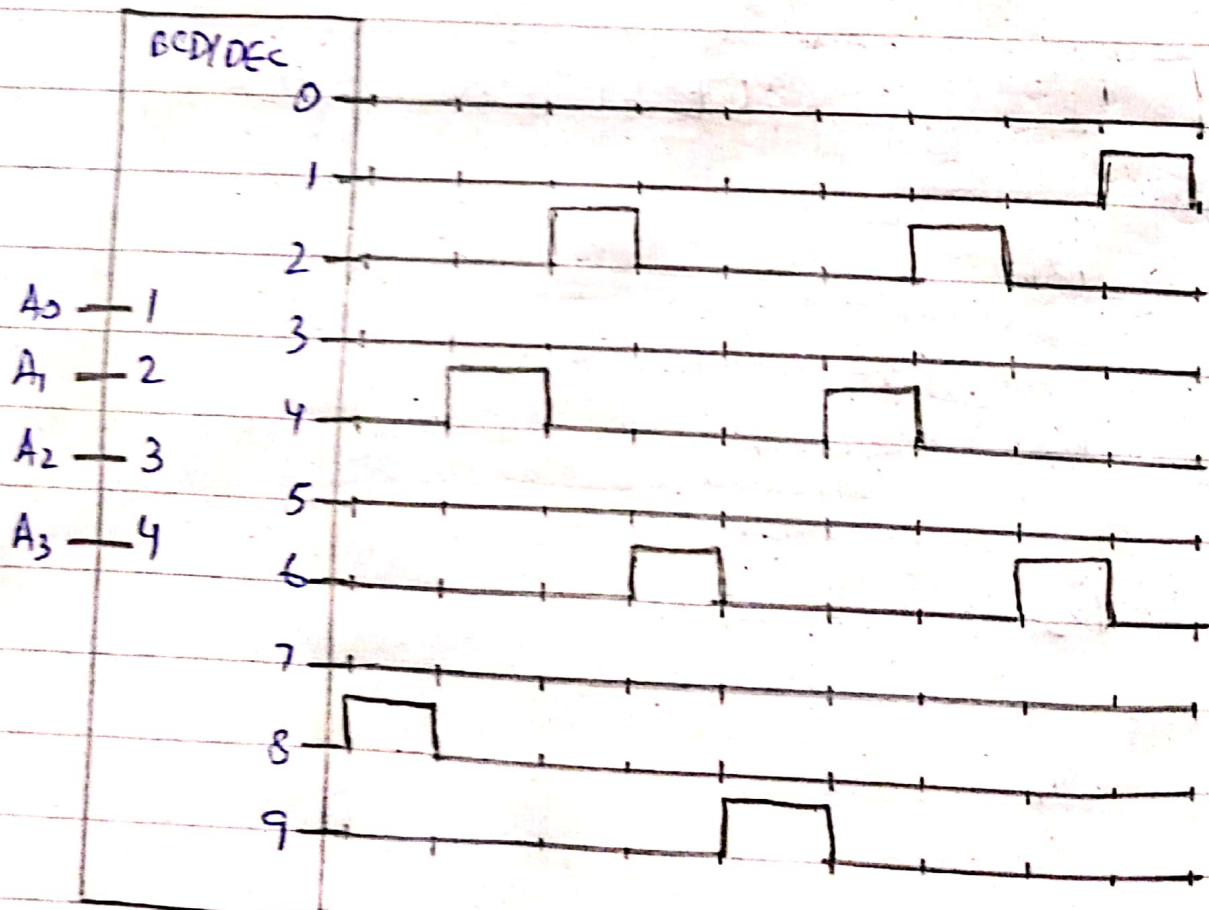

QUESTION G:

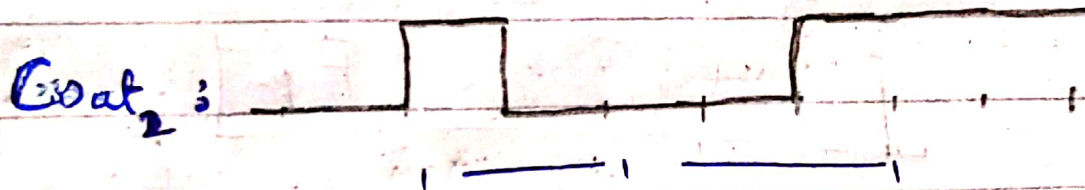


QUESTION

QUESTION H

D_0




D_1

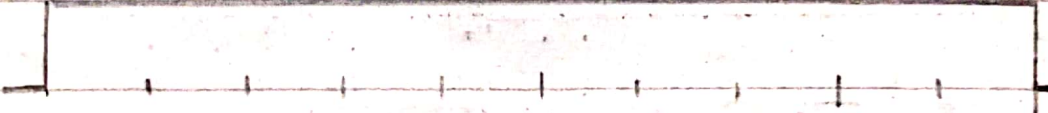

D_2



D_3

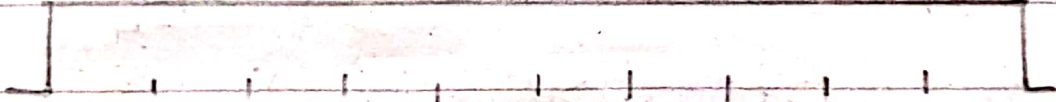



S_0




S_1



Output

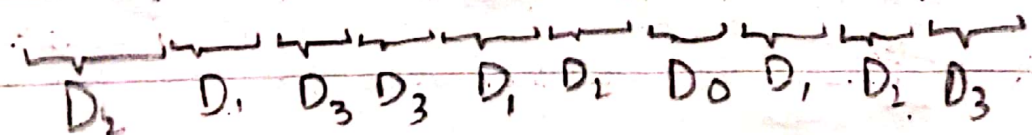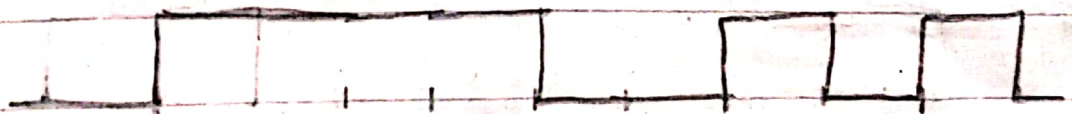

QUESTION I

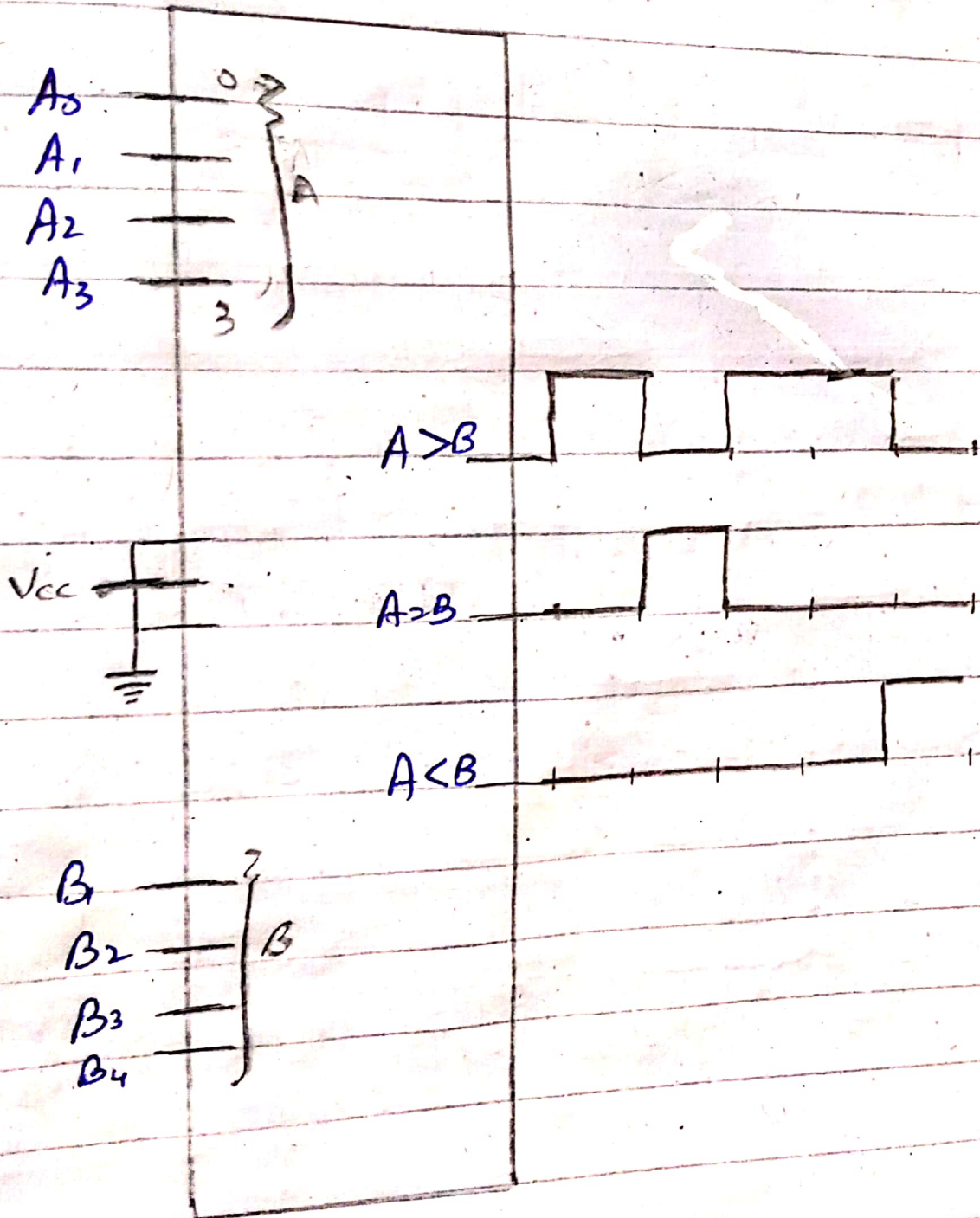

QUESTION 5

i)

$$X = (A+B)' \cdot (C \cdot D)$$

$$A=0; B=0; C=1; D=1$$

ii)

Boolean expression such that the "low" state of the circuit activates the alarm.

$$X = ((A' \cdot B') \cdot (C \cdot D))'$$

Input condition which activate the alarm.

$$A=0$$

$$B=0$$

$$C=1$$

$$D=1$$