

A decorative graphic on the left side of the slide, consisting of a network of white lines and circles on a blue gradient background. The lines are vertical and horizontal, with some diagonal segments, and the circles are of varying sizes, resembling a circuit board or a digital network.

# DIGITAL LOGIC DESIGN

## EE(227)

The background is a blue gradient with white circuit-like lines and circles in the corners. The text is centered in a white serif font.

# Chapter No:8

## Shift Registers

The background is a blue gradient with white circuit-like lines in the corners. These lines consist of straight segments and small circles, resembling a stylized PCB or electronic schematic.

# Outlines

Shift Register Operations

Types of Shift Register Data I/Os

Bidirectional Shift Registers

Shift Register Counters



Shift Register Applications

## BASIC SHIFT REGISTER FUNCTIONS


A **register** is a digital circuit with two basic functions: data storage and data movement. The storage capability of a register makes it an important type of memory device.

A register can consist of one or more flip-flops used to store and shift data.


### The flip-flop as a storage element.

  

 
Basic data movement in shift registers. (Four bits are used for illustration. The bits move in the direction of the arrows.)




(a) Serial in/shift right/serial out

 


(b) Serial in/shift left/serial out

 


(c) Parallel in/serial out

 


(d) Serial in/parallel out

 

(e) Parallel in/parallel out

 

(f) Rotate right

 


(g) Rotate left



 
# SERIAL IN/SERIAL OUT SHIFT REGISTERS




The serial in/serial out shift register accepts data serially—that is, one bit at a time on a single line. It produces the stored information on its output also in serial form.


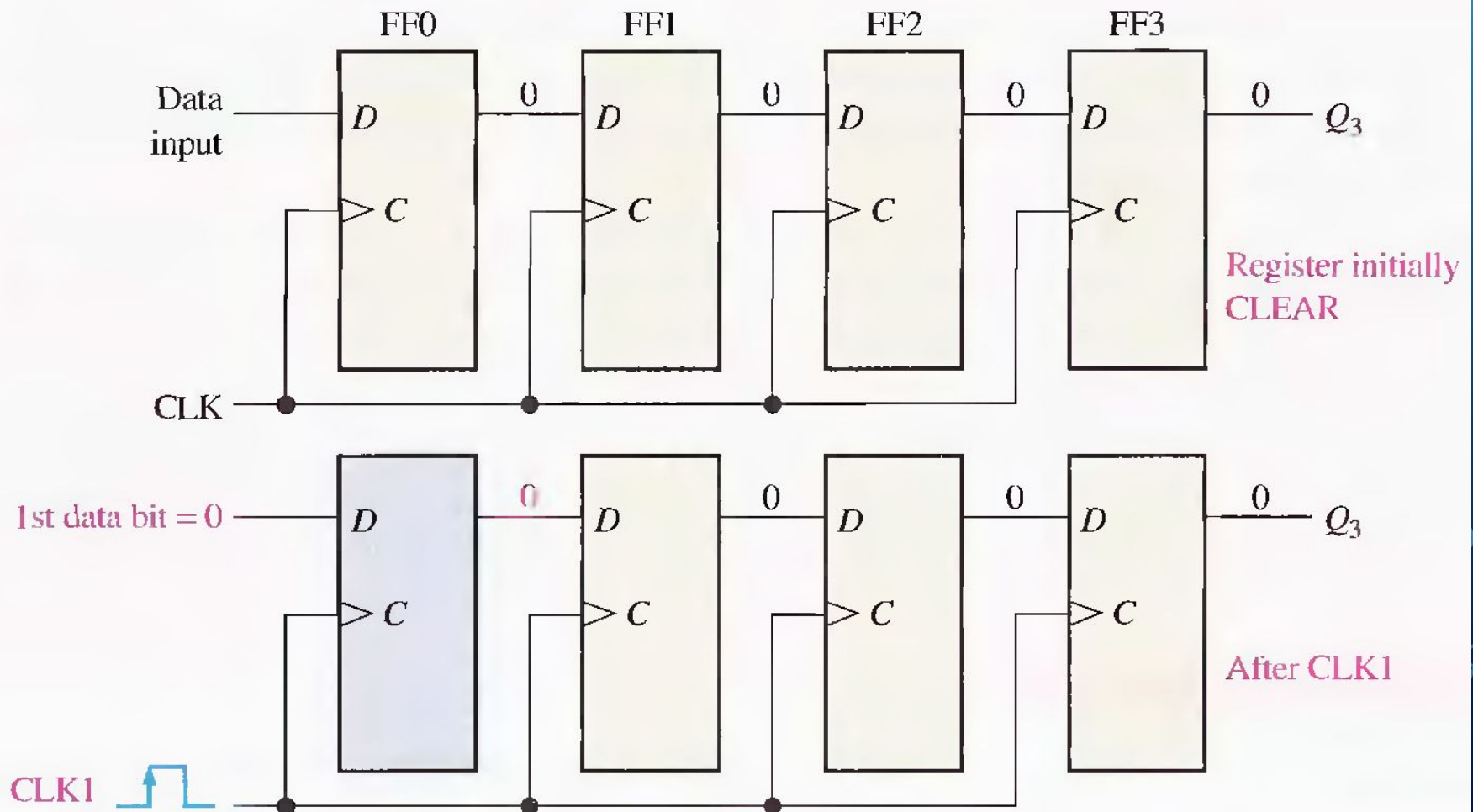
# Four bits (1010) being entered serially into the register.




For serial data, one bit at a time is transferred.




   





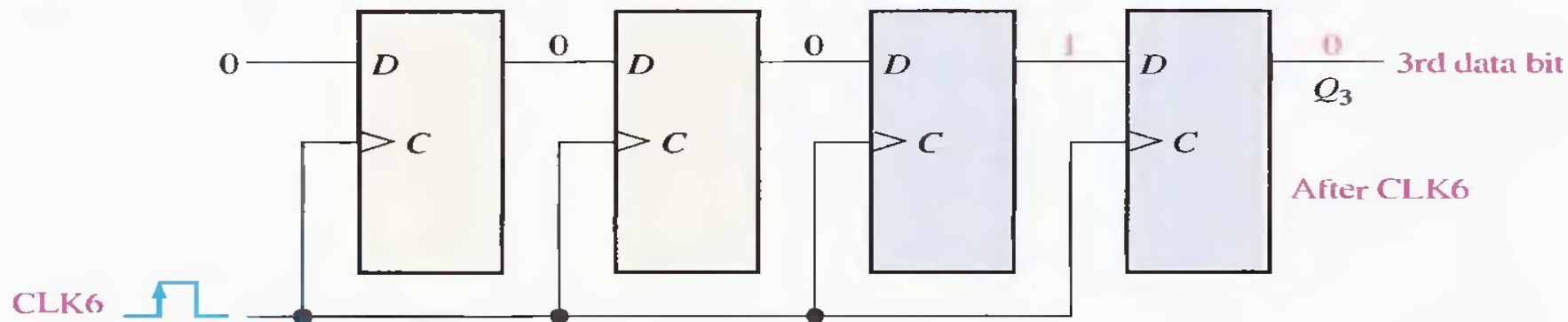  Four bits (1010) being serially shifted out of the register and replaced by all zeros.





 

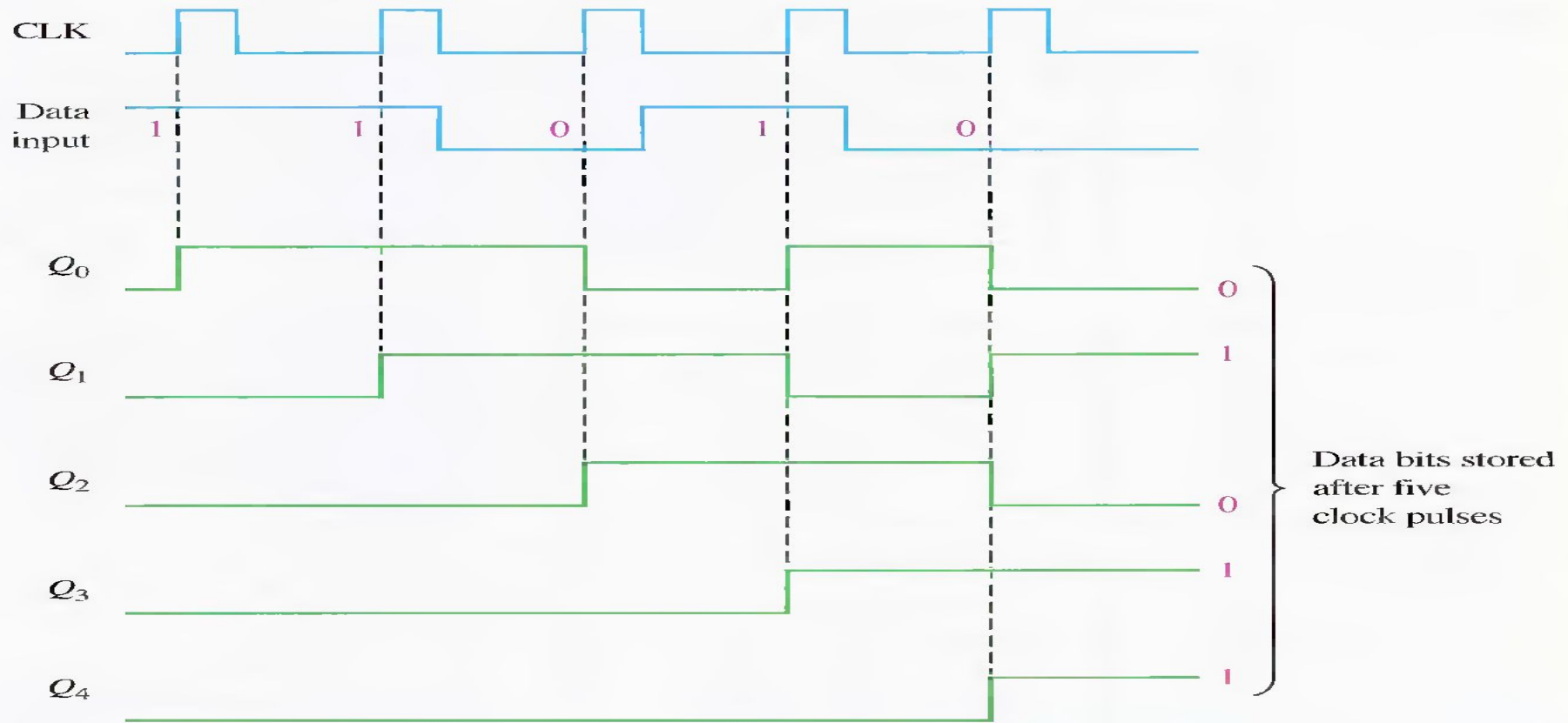 Show the states of the 5-bit register in Figure, for the specified data input and clock waveforms. Assume that the register is initially cleared (all 0s).





# SERIAL IN/PARALLEL OUT SHIFT REGISTERS

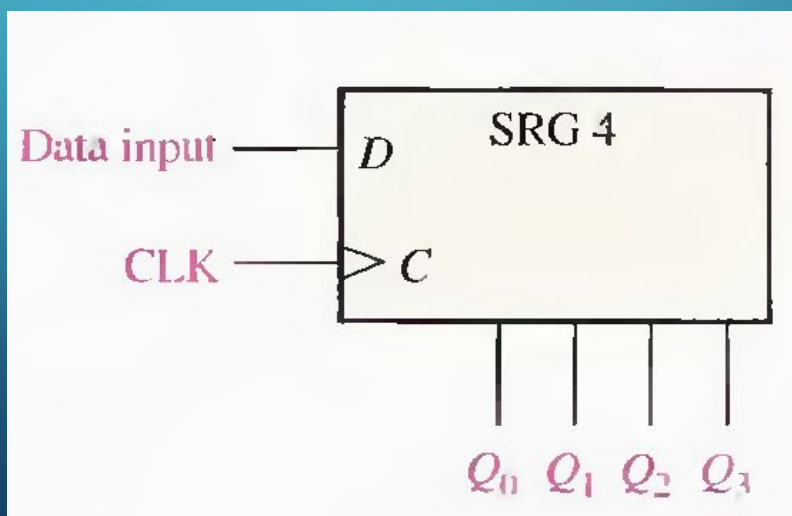 



Show the states of the 4-bit register (SRG 4) for the data input and clock waveforms in Figure 9–9(a). The register initially contains all 1s.

  
The register contains 0110 after four clock pulses. See Figure 9–9(b).






  
# THE 74HC164 8-BIT SERIAL IN/PARALLEL OUT SHIFT REGISTER




 

# PARALLEL IN/SERIAL OUT SHIFT REGISTERS

 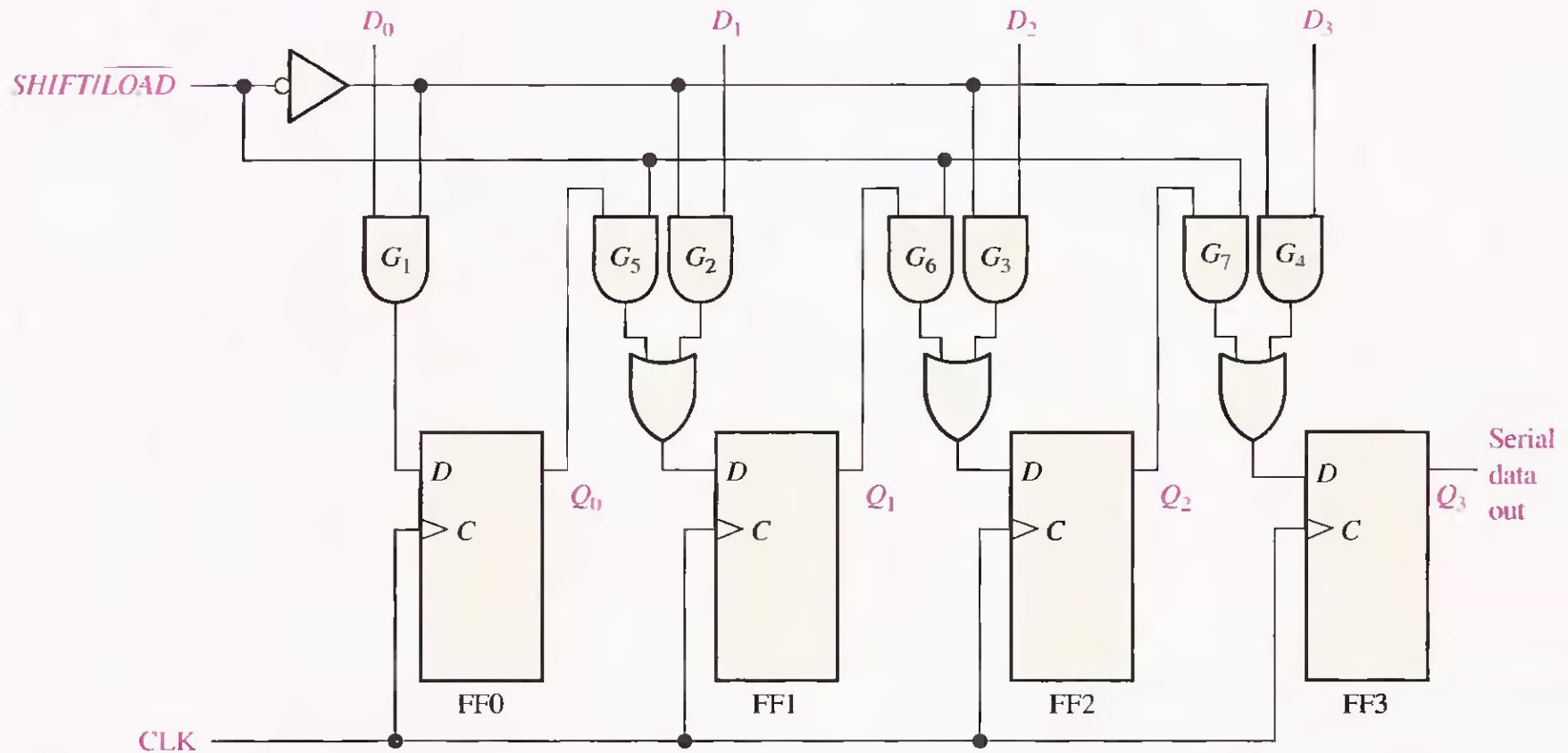


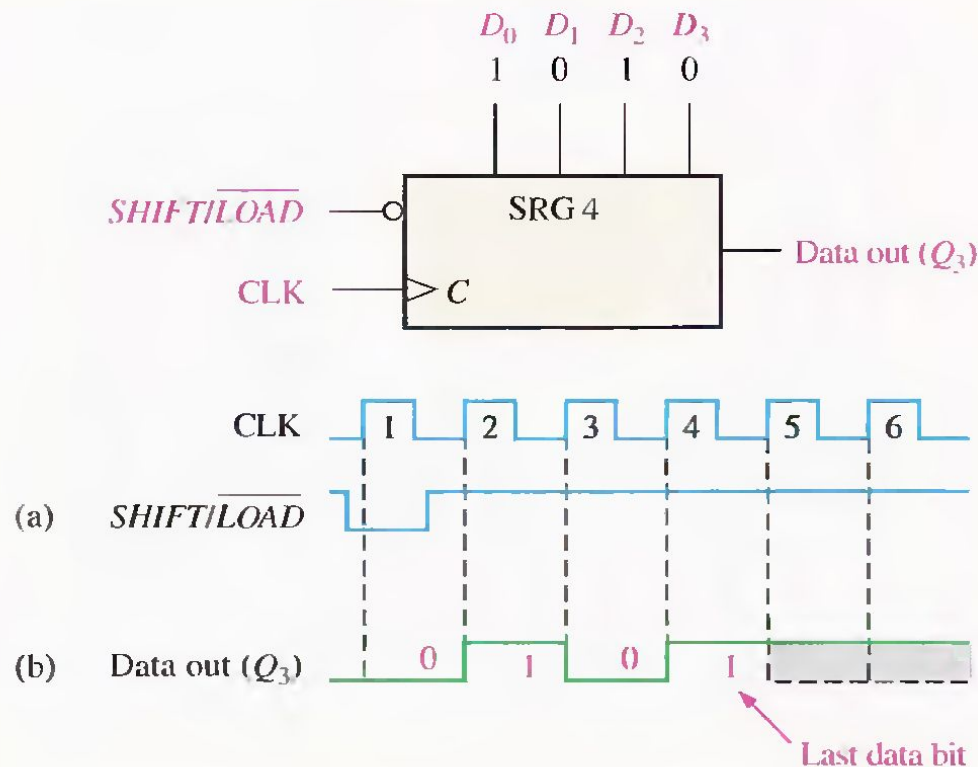
Show the data-output waveform for a 4-bit register with the parallel input data and the clock and *SHIFT/LOAD* waveforms given in Figure 9–13(a). Refer to Figure 9–12(a) for the logic diagram.




On clock pulse 1, the parallel data ( $D_0D_1D_2D_3 = 1010$ ) are loaded into the register, making  $Q_3$  a 0. On clock pulse 2 the 1 from  $Q_2$  is shifted onto  $Q_3$ ; on clock pulse 3 the 0 is shifted onto  $Q_3$ ; on clock pulse 4 the last data bit (1) is shifted onto  $Q_3$ ; and on clock pulse 5, all data bits have been shifted out, and only 1s remain in the register (assuming the  $D$  input remains a 1). See Figure 9–13(b).



  
# THE 74HC165 8-BIT PARALLEL LOAD SHIFT REGISTER





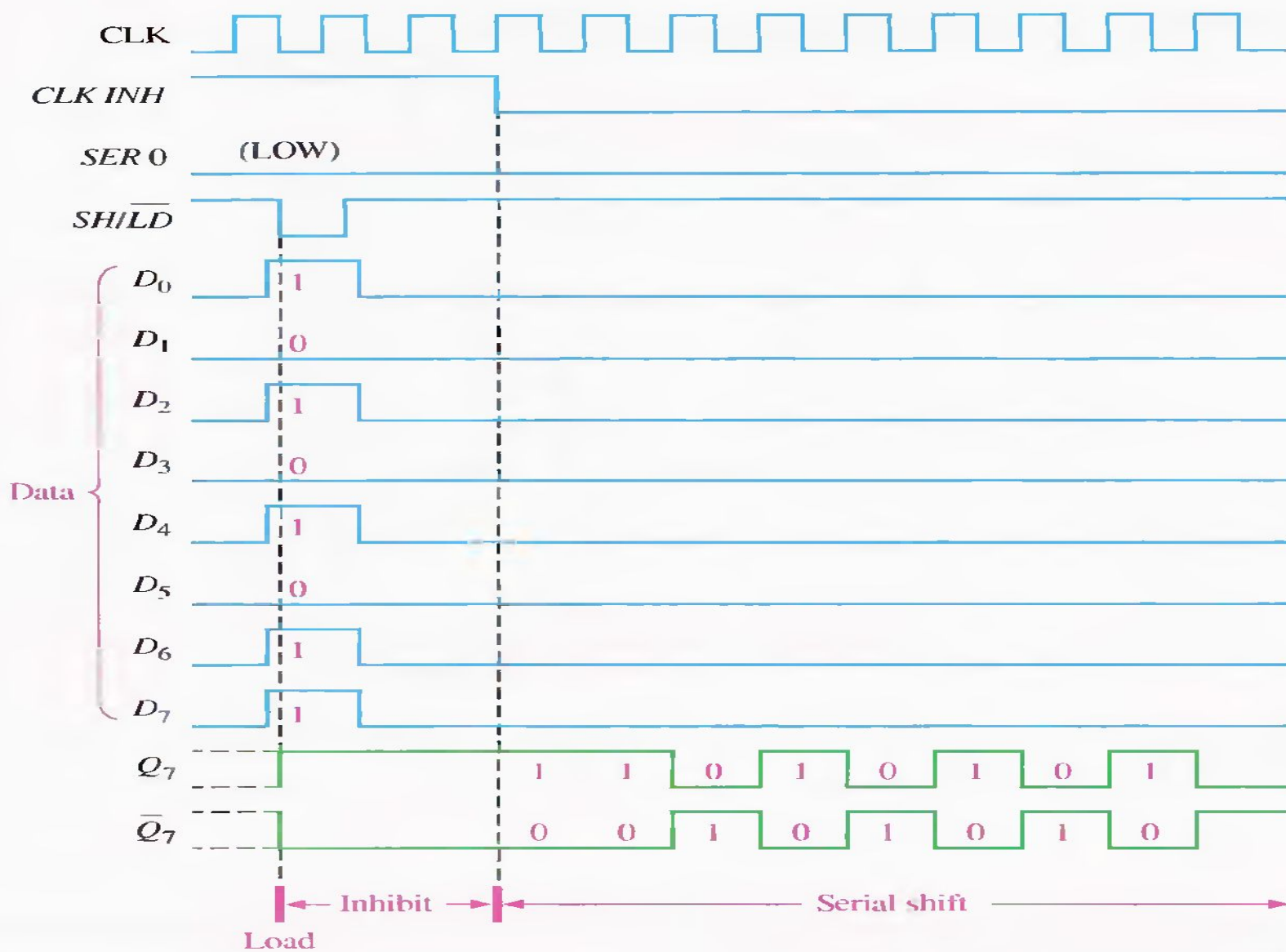

 
# PARALLEL IN/PARALLEL OUT SHIFT REGISTERS


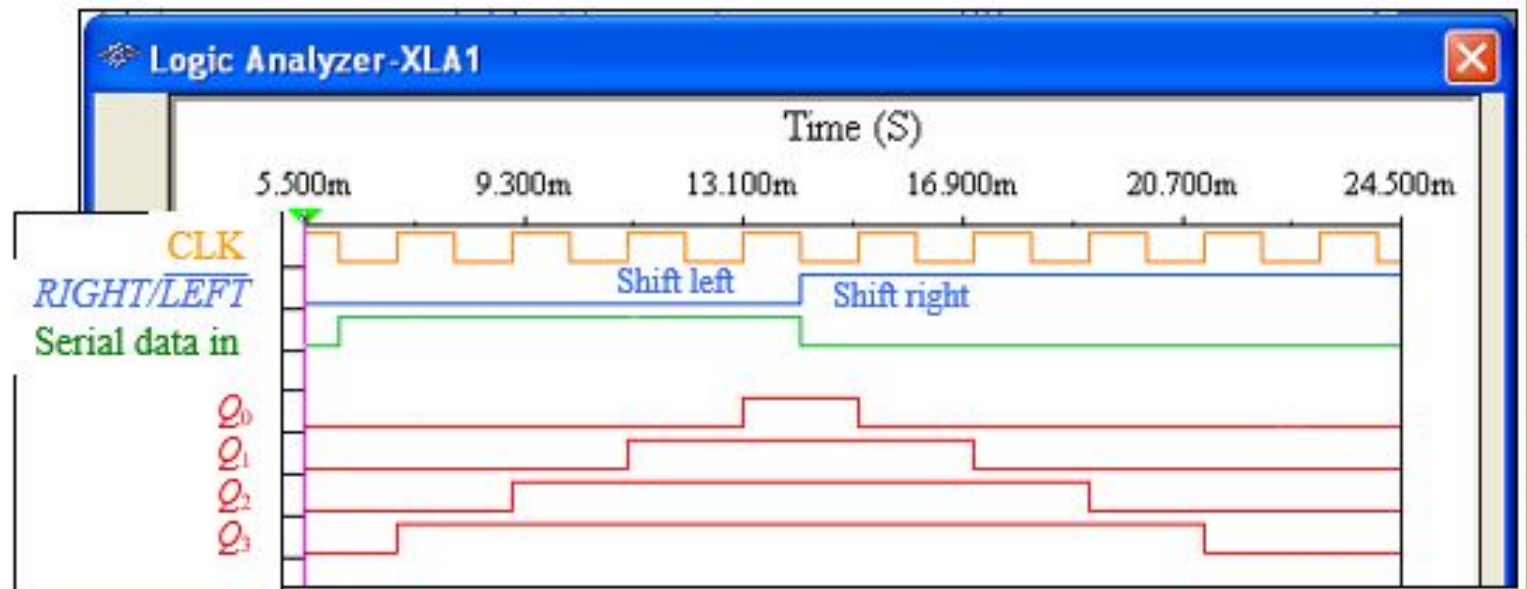
## Bidirectional Shift Register

Bidirectional shift registers can shift the data in either direction using a *RIGHT/LEFT* input.

The logic analyzer simulation shows a bidirectional shift register such as the one shown in Figure 9-19 of the text. Notice the HIGH level from the Serial data in is shifted at first from  $Q_3$  toward  $Q_0$ .



## Bidirectional Shift Register

**Question**

How will the pattern change if the *RIGHT/LEFT* control signal is inverted?

**Answer**


See display



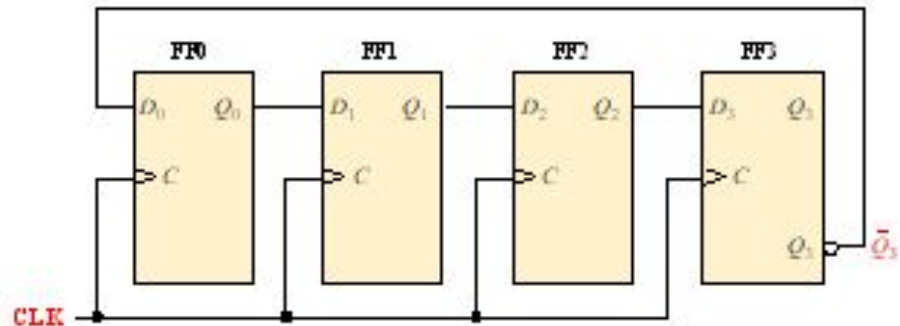
## Shift Register Counters

Shift registers can form useful counters by recirculating a pattern of 0's and 1's. Two important shift register counters are the *Johnson counter* and the *ring counter*.

The Johnson counter can be made with a series of D flip-flops



 
... or with a series of J-K flip flops. Here  $Q_3$  and  $\bar{Q}_3$  are fed back to the  $J$  and  $K$  inputs with a “twist”.




 
## Johnson Counter

Redrawing the same Johnson counter (without the clock shown) illustrates why it is sometimes called as a “twisted-ring” counter.



## Johnson Counter

The Johnson counter is useful when you need a sequence that changes by only one bit at a time but it has a limited number of states ( $2n$ , where  $n$  = number of stages).

The first five counts for a 4-bit Johnson counter that is initially cleared are:

CLK	$Q_0$	$Q_1$	$Q_2$	$Q_3$
0	0	0	0	0
1	1	0	0	0
2	1	1	0	0
3	1	1	1	0
4	1	1	1	1

### Question

What are the remaining 3 states?

**TABLE 8-3**

Four-bit Johnson sequence.

Clock Pulse	$Q_0$	$Q_1$	$Q_2$	$Q_3$
0	0	0	0	0
1	1	0	0	0
2	1	1	0	0
3	1	1	1	0
4	1	1	1	1
5	0	1	1	1
6	0	0	1	1
7	0	0	0	1

**TABLE 8-4**


Five-bit Johnson sequence.

Clock Pulse	$Q_0$	$Q_1$	$Q_2$	$Q_3$	$Q_4$
0	0	0	0	0	0
1	1	0	0	0	0
2	1	1	0	0	0
3	1	1	1	0	0
4	1	1	1	1	0
5	1	1	1	1	1
6	0	1	1	1	1
7	0	0	1	1	1
8	0	0	0	1	1
9	0	0	0	0	1

 
## Ring Counter

The ring counter can also be implemented with either D flip-flops or J-K flip-flops.

Here is a 4-bit ring counter constructed from a series of D flip-flops. Notice the feedback.



 Like the Johnson counter, it can also be implemented with J-K flip flops.




## Ring Counter

Redrawing the Ring counter (without the clock shown) shows why it is a “ring”.

The disadvantage to this counter is that it must be preloaded with the desired pattern (usually a single 0 or 1) and it has even fewer states than a Johnson counter ( $n$ , where  $n$  = number of flip-flops).

 On the other hand, it has the advantage of being self-decoding with a unique output for each state.







## Ring Counter

CLK

$Q_0$

$Q_1$

$Q_2$

$Q_3$

$Q_4$

$Q_5$

$Q_6$

$Q_7$